
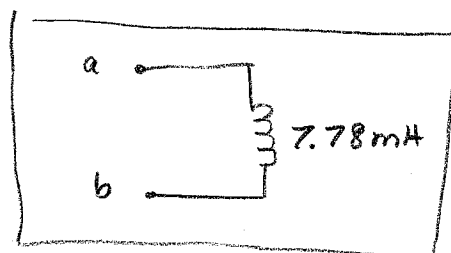
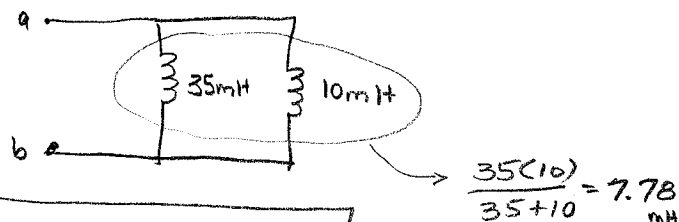
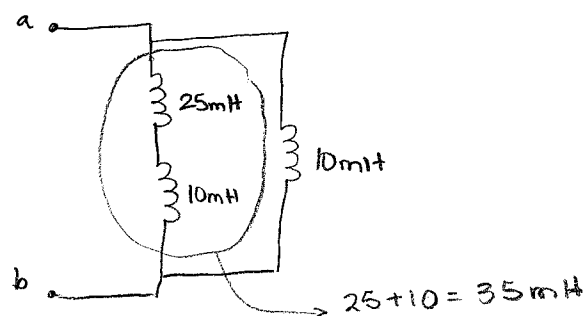


Key

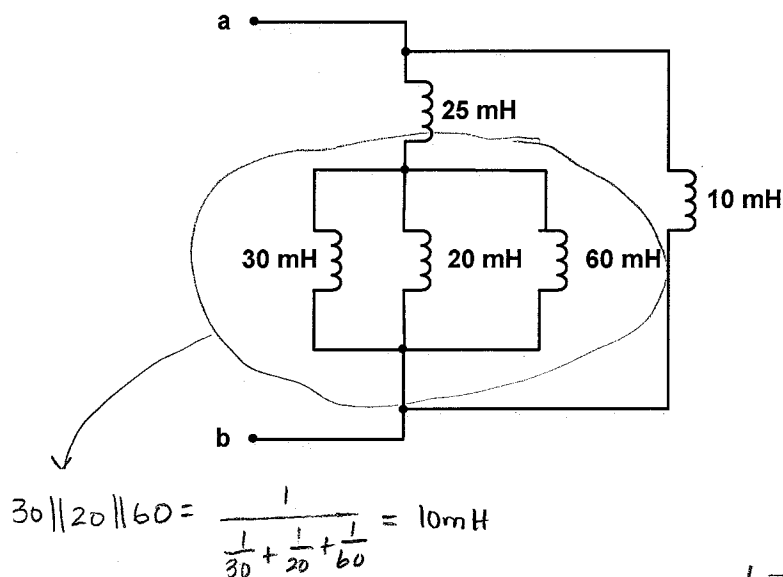1. Simplify the following to a single equivalent component. (6 pts)




2. If the voltage across a 2-mH inductor is $v(t) = 2\cos(3t)$ V, find the current through the inductor as a function of t if the initial current at $t=0$ is 0.25 A. (4 pts)

$$\begin{aligned} i(t) &= v(0) + \frac{1}{L} \int_0^t v \, d\lambda = 0.25 + \frac{1}{0.002} \int_0^t 2 \cos(3\lambda) \, d\lambda \\ &= 0.25 + 500 \left(\frac{2}{3} \right) \sin(3\lambda) \Big|_0^t = \boxed{0.25 + \frac{1000}{3} \sin(3t) \text{ A}} \end{aligned}$$

3. If the current through a 4- μ H inductor is $i(t) = 2e^{-5t}$ A, find the voltage across the inductor as a function of t . (4 pts)

$$\begin{aligned} v &= L \frac{di}{dt} = (4 \times 10^{-6}) (-10e^{-5t}) \\ &= \boxed{-4 \times 10^{-5} e^{-5t} \text{ V}} \end{aligned}$$

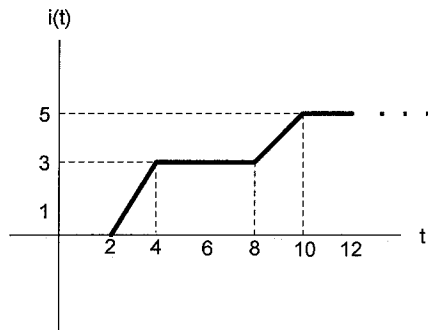
4. If the current through a 0.25-H inductor is given by the graph below, find the piecewise function that describes the voltage across the inductor and sketch the graph of the voltage. (6 pts)



$$v = L \frac{di}{dt}$$

$$\frac{di}{dt} = \begin{cases} 0 & , & 0 < t < 2 \\ 3/2 & , & 2 < t < 4 \\ 0 & , & 4 < t < 8 \\ 1 & , & 8 < t < 10 \\ 0 & , & t > 10 \end{cases}$$
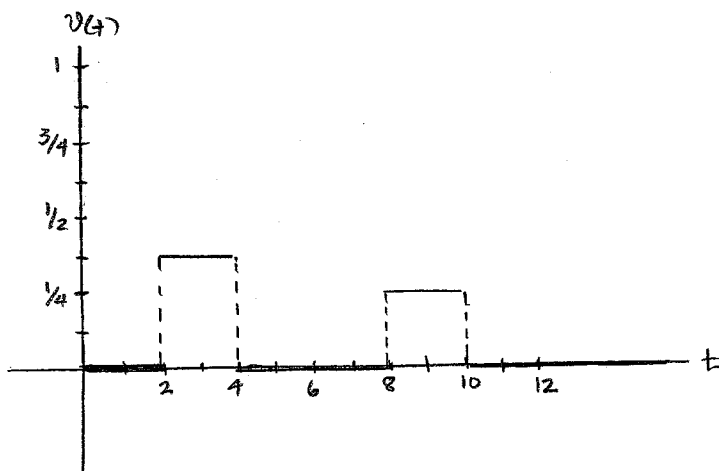
$$v = \begin{cases} 0 & , & 0 < t < 2 \\ 3/8 & , & 2 < t < 4 \\ 0 & , & 4 < t < 8 \\ 1/4 & , & 8 < t < 10 \\ 0 & , & t > 10 \end{cases}$$




Key

EE281B


Homework #11 -- 20 points

Due: Friday, October 8, 2010

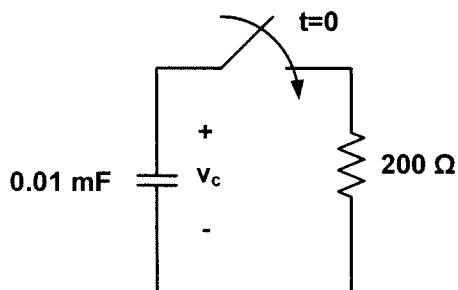
1. If the initial voltage across the capacitor is $v_c(0) = 45\text{V}$, find the time (in seconds) for the voltage v_c to be reduced to 10 V as the capacitor discharges. (7 pts)



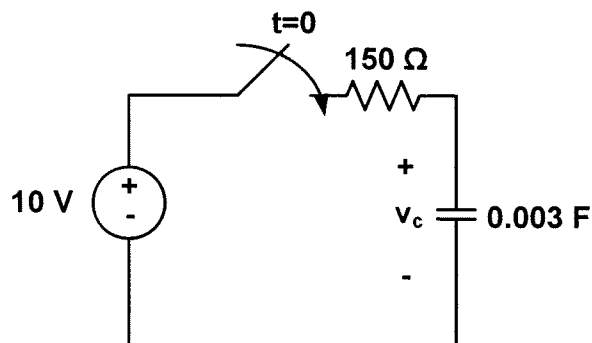
2. Consider the RC circuit in which v_c is the capacitor voltage.



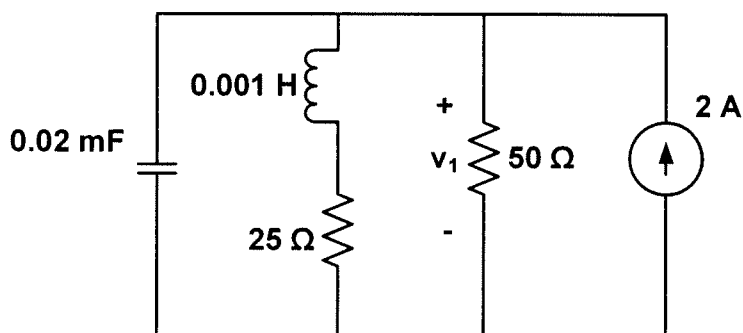- a. Write the differential equation in standard form used to find $v_c(t)$ for $t > 0$. (3 pts)
- b. If $v(0^+) = 0\text{ V}$, find the solution of the differential equation (5 pts)
3. Solve the steady-state voltage v_1 in the following circuit. (5 pts)



EE281 Homework #11

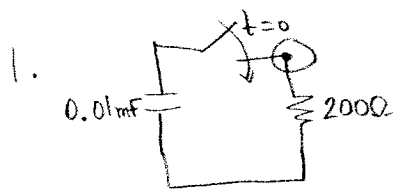

$$RC = (0.01 \times 10^{-3})(200) = 0.002$$

$$v_c(0^+) = 45V$$

$$C \frac{dv_c}{dt} + \frac{v_c}{R} = 0$$

$$\frac{dv_c}{dt} + \frac{1}{RC} v_c = 0$$

$$\frac{dv_c}{dt} + 500 v_c = 0$$

$$\lambda + 500 = 0$$

$$\lambda = -500$$

$$v_c(t) = K e^{-500t}$$

$$v_c(0) = 45 = K e^0$$

$$K = 45$$


$$v_c(t) = 45 e^{-500t} V$$

$$10 = 45 e^{-500t}$$

$$\ln\left(\frac{10}{45}\right) = -500t$$

$$t = -\frac{1}{500} \ln\left(\frac{10}{45}\right)$$

$$t = 3.01 \text{ ms}$$

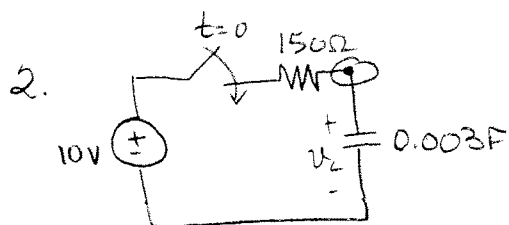

$$v(0^+) = 0 V$$

$$0.003 \frac{dv_c}{dt} + \frac{v_c - 10}{150} = 0$$

$$\frac{dv_c}{dt} + \frac{1}{0.45} v_c = \frac{10}{0.45}$$

$$a) \quad \frac{dv_c}{dt} + 2.22 v_c = 22.22$$

$$b) \quad \frac{dv_c}{dt} + 2.22 v_c = 0$$

$$\lambda + 2.22 = 0$$

$$\lambda = -2.22$$

$$v_c = K_1 e^{-2.22t}$$

$$v_p = K_2$$

$$0 + 2.22 K_2 = 22.22$$


$$K_2 = 10$$

$$v_c = K_1 e^{-2.22t} + 10$$


$$v_c(0^+) = 0 = K_1 e^0 + 10$$

$$K_1 = -10$$

$$v_c(t) = 10 - 10 e^{-2.22t} V$$

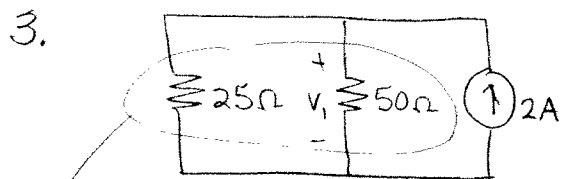


$$25 \parallel 50 = \frac{50}{3}$$

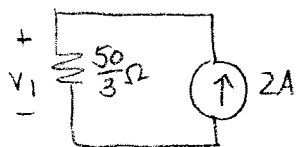


$$V_1 = \frac{50}{3} (2A) = \frac{100}{3} V$$

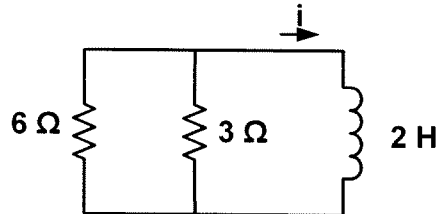
1. Consider the source-free RL circuit in which i is the inductor current.



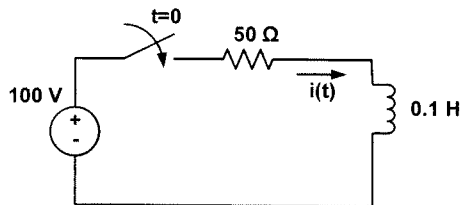- Write the differential equation in standard form used to find $i(t)$ for $t > 0$. (4 pts)
 - If $i(0^+) = 2\ \text{A}$, find the solution of the differential equation (i.e. the natural response of the circuit). (4 pts)
 - What is the time constant, τ , for this problem? (2 pts)
2. Consider the circuit shown below.



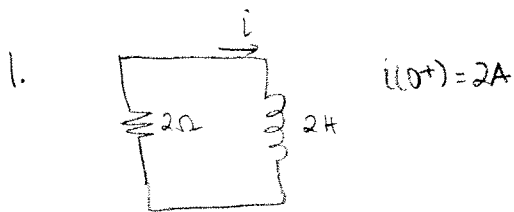- What is the initial current in the loop, $i(0^+)$? (2 pts)
- Find the current, i , for $t > 0$ as a function of t . (8 pts)



a) KVL: $L \frac{di}{dt} + Ri = 0$

$$\frac{di}{dt} + \frac{R}{L} i = 0$$

$$\boxed{\frac{di}{dt} + i = 0}$$

b) $\lambda + 1 = 0$
 $\lambda = -1$


$$i(t) = K e^{-t}$$

$$i(0^+) = 2 = K e^0$$

$$K = 2$$

$$\boxed{i(t) = 2e^{-t} A}$$

c) $\boxed{\tau = \frac{L}{R} = 1s}$

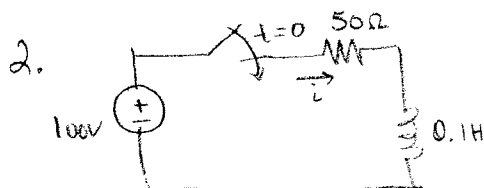

a) $\boxed{i(0^+) = 0 A}$

b) KVL: $-100 + 50i + 0.1 \frac{di}{dt} = 0$

$$\frac{di}{dt} + 500i = 1000$$

$$\frac{di}{dt} + 500i = 0$$

$$i_h = K_1 e^{-500t}$$

$$i_p = K_2 \quad \text{plug into D.E.}$$

$$0 + 500 K_2 = 1000$$

$$K_2 = 2$$

$$i(t) = K_1 e^{-500t} + 2$$


$$i(0^+) = 0 = K_1 e^0 + 2$$

$$K_1 = -2$$

$$\boxed{i(t) = 2 - 2e^{-500t} A}$$

can use the form of the eqn given in the text rather than solving the D.E.

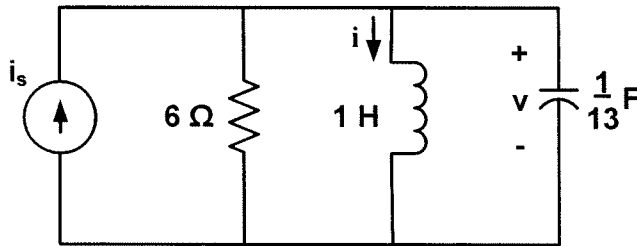1. In the following circuit $i_s = 250e^{-2t}$ V for $t > 0$.



- Write a KCL equation at the top node and then take the derivative to create a differential equation in terms of the voltage, v . (4 pts)
- What are the initial current, $i(0^+)$, and initial voltage, $v(0^+)$, if the source has been off for a long time and is then turned on at $t=0$? (2 pts)
- Find the form of the source-free response (do not solve for the constants). (4 pts)
- Find the particular response, $v_p(t)$. (4 pts)
- Find the complete solution, $v(t)$. (Solve for all constants.) (4 pts)
- Is the circuit overdamped, underdamped, or critically damped? (2 pts)

EE281 Hwk 13

$$1. a) -i_s + \frac{V}{6} + \frac{1}{L} \int_{-\infty}^t V d\lambda + \frac{1}{13} \frac{dV}{dt} = 0$$

$$i_s = 250e^{-2t} A$$

$$\frac{di_s}{dt} = -500e^{-2t} A$$

$$\boxed{\frac{d^2V}{dt^2} + \frac{13}{6} \frac{dV}{dt} + 13V = -500e^{-2t}}$$

$$b) \begin{cases} i(0^+) = 0 \\ V(0^+) = 0 \end{cases}$$

$$c) \frac{d^2V}{dt^2} + \frac{13}{6} \frac{dV}{dt} + 13V = 0$$

$$\Delta^2 + \frac{13}{6} \Delta + 13 = 0$$

$$\Delta = \frac{-\frac{13}{6} \pm \sqrt{(\frac{13}{6})^2 - 4(13)}}{2} = -1.08 \pm j 3.44$$

$$\boxed{V_h(t) = K_1 e^{-1.08t} \cos(3.44t) + K_2 e^{-1.08t} \sin(3.44t)}$$

$$d) V_p(t) = Ae^{-2t}$$

$$V_p' = -2Ae^{-2t}$$

$$V_p'' = 4Ae^{-2t}$$

$$4Ae^{-2t} + \frac{13}{6}(-2Ae^{-2t}) + 13(Ae^{-2t}) = -500e^{-2t}$$

$$4A - \frac{13}{3}A + 13A = -500$$

$$A = -500 / (4 - \frac{13}{3} + 13) = -39.47$$

$$\boxed{V_p(t) = -39.47 e^{-2t}}$$

$$e) V(t) = K_1 e^{-1.08t} \cos(3.44t) + K_2 e^{-1.08t} \sin(3.44t) - 39.47 e^{-2t}$$

$$V(0^+) = 0 = K_1 - 39.47$$

$$K_1 = 39.47$$

$$i(0) = 0 \rightarrow \frac{dV}{dt} = 0$$

$$V'(t) = K_1 e^{-1.08t} (-3.44 \sin(3.44t)) - 1.08 K_1 e^{-1.08t} \cos(3.44t) + K_2 e^{-1.08t} (3.44 \cos(3.44t)) - 1.08 K_2 e^{-1.08t} \sin(3.44t) + 78.94 e^{-2t}$$

$$V'(0) = 0 = -1.08 K_1 + 3.44 K_2 + 78.94$$

$$K_2 = (1.08(39.47) - 78.94) / 3.44 = -10.56$$

$$\boxed{V(t) = 39.47 e^{-1.08t} \cos(3.44t) - 10.56 e^{-1.08t} \sin(3.44t) - 39.47 e^{-2t} V}$$

f) underdamped

Key

EE281 B

Homework #14 -- 20 points


Due: Friday, October 22, 2010

1. Find the RMS value of each of the following signals. (4 pts each)

a. $i(t) = 8 \sin(500t - 15^\circ) \text{ A}$

$$I_{\text{rms}} = \frac{8}{\sqrt{2}} \text{ A}$$

b.

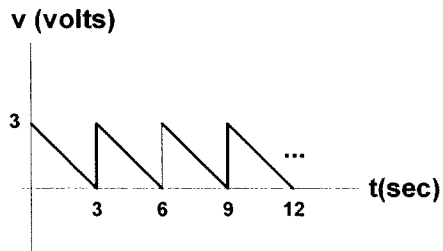

$$V_{\text{rms}} = \sqrt{\frac{1}{3} \int_0^3 (3-t)^2 dt} = \sqrt{\frac{1}{3} \left[-\frac{1}{3} (3-t)^3 \right]_0^3} = \sqrt{-\frac{1}{9} (0 - 3^3)} = \sqrt{\frac{27}{9}} = \sqrt{3} \text{ V}$$

2. Write each of the following signals as phasors. (3 pts each)


a. $v(t) = 12 \cos(4t + 12^\circ) \text{ V}$

$$V = 12 \angle 12^\circ \text{ V}$$

b. $i(t) = 1.4 \sin(20t + 30^\circ) \text{ A}$
 $= 1.4 \cos(20t - 60^\circ) \text{ A}$


$$I = 1.4 \angle -60^\circ \text{ A}$$

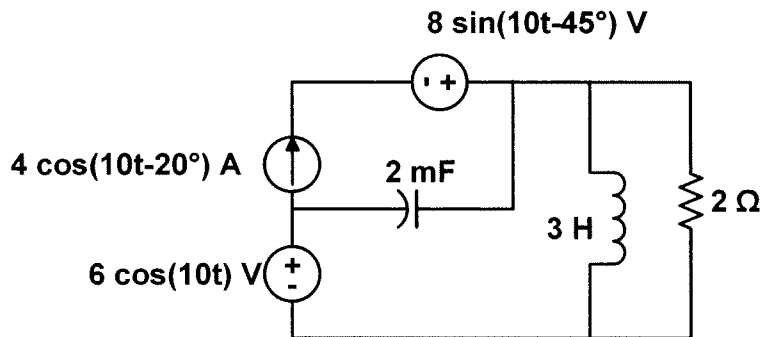3. Redraw the following circuit in the frequency domain (in terms of phasors and impedances). (6 pts)




$$\frac{1}{j\omega C} = -j \frac{1}{(2 \times 10^{-3})(10)} = -j50$$


$$j\omega L = j(10)(3) = j30$$

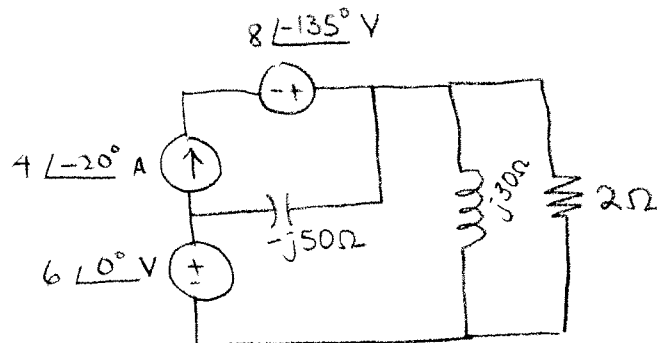

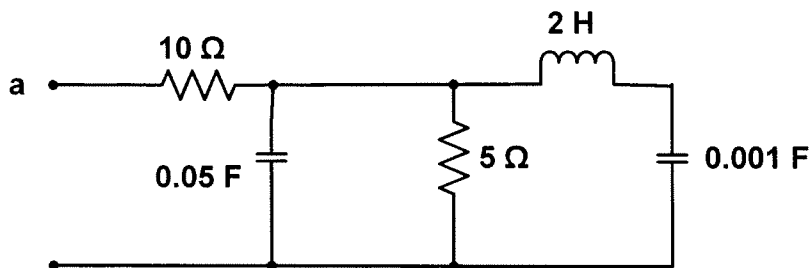
1. Write the following as a single impedance. Assume that $\omega=100$ rad/sec. (6 pts)



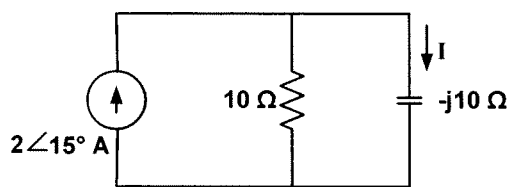2. Find the steady-state current $i(t)$ in the following circuit if $\omega=100$ rad/sec. (7 pts)





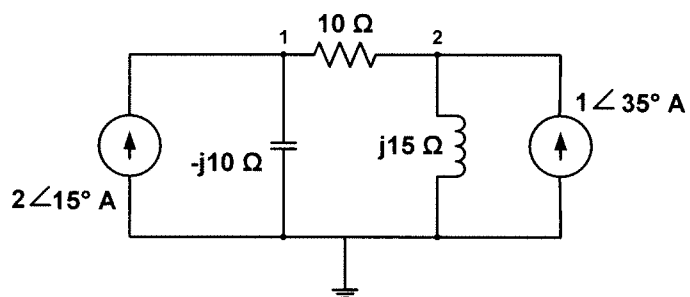3. Set up the node voltage equations in matrix form for the following circuit. (7 pts)





Homework #15

$$\omega = 100 \text{ rad/sec.}$$

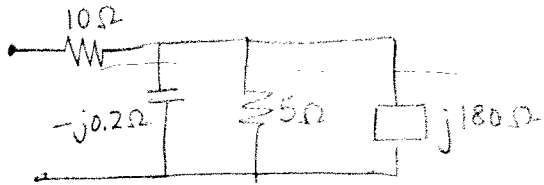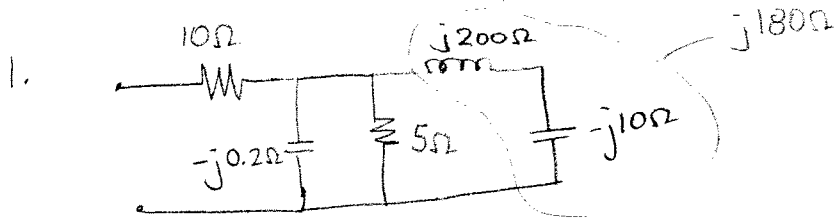

$$\frac{1}{\frac{1}{-j0.2} + \frac{1}{5} + \frac{1}{j180}} = 0.2 \angle -87.71^\circ \Omega$$

$$= 0.008 - j0.2 \Omega$$

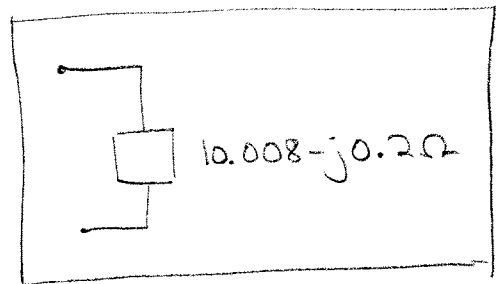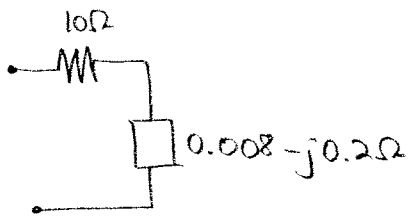

$$= 10.0 \angle -1.14^\circ \Omega$$

2. Current divider:

$$I = \frac{10}{10 - j10} (2 \angle 15^\circ) = 1.414 \angle 60^\circ \text{ A}$$

$$i(t) = 1.414 \cos(100t + 60^\circ) \text{ A}$$

3. node 1

$$-2 \angle 15^\circ + \frac{V_1}{-j10} + \frac{V_1 - V_2}{10} = 0$$

$$(1) \left(\frac{1}{10} + j\frac{1}{10} \right) V_1 - \frac{1}{10} V_2 = 2 \angle 15^\circ$$


node 2

$$\frac{V_2 - V_1}{10} + \frac{V_2}{j15} - 1 \angle 35^\circ = 0$$

$$(2) -\frac{1}{10} V_1 + \left(\frac{1}{10} - j\frac{1}{15} \right) V_2 = 1 \angle 35^\circ$$


$$\begin{bmatrix} \frac{1}{10} + j\frac{1}{10} & -\frac{1}{10} \\ -\frac{1}{10} & \frac{1}{10} - j\frac{1}{15} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2 \angle 15^\circ \\ 1 \angle 35^\circ \end{bmatrix}$$

1. Given the following circuit, find:

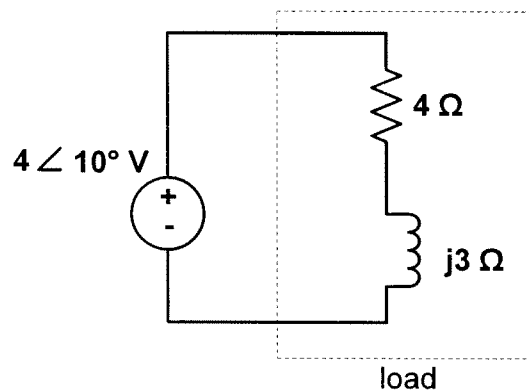

- The average power absorbed by the load. (4 pts)
 - The reactive power absorbed by the load. (4 pts)
 - The apparent power absorbed by the load. (3 pts)
 - The power factor of the load. (3 pts)
 - Sketch the power triangle for the load. (3 pts)
2. What is the purpose of the large capacitor banks often found in factories which operate large induction motors? (3 pts)

Home work #16

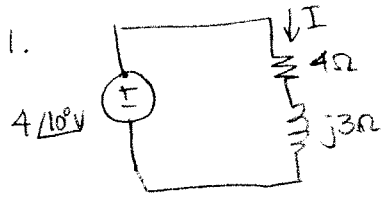

$$Z = 4 + j3 \Omega = 5 \angle 36.87^\circ \Omega$$

$$I = \frac{V}{Z} = \frac{4 \angle 10^\circ}{4 + j3} = 0.8 \angle -26.87^\circ \text{ A}$$


$$a) P = \frac{1}{2} V_m I_m \cos \theta = \frac{1}{2} (4) (0.8) \cos (36.87^\circ) = \boxed{1.28 \text{ W}}$$

$$b) Q = \frac{1}{2} V_m I_m \sin \theta = \frac{1}{2} (4) (0.8) \sin (36.87^\circ) = \boxed{0.96 \text{ VAR}}$$

$$c) AP = \frac{P}{PF} = \frac{1.28}{\cos(36.87^\circ)} = \boxed{1.6 \text{ VA}}$$

$$d) PF = \cos \theta = \boxed{0.8 \text{ lagging}}$$

e)

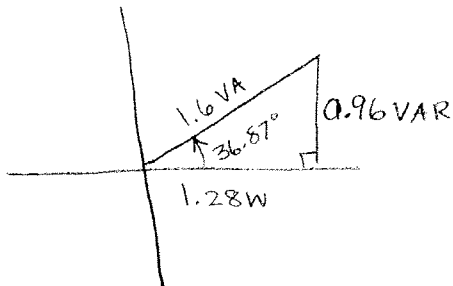


(Other formulas for P , Q + AP are also correct)


2. Power factor correction

This makes the load look more resistive by counteracting the positive reactive power of the motors with a negative reactive power from the capacitors.

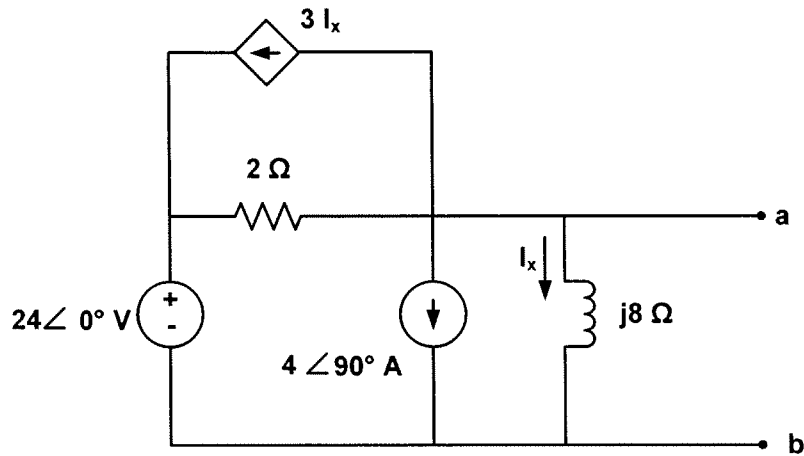1. Find the Thévenin and Norton equivalents of the following circuit. (8 pts)




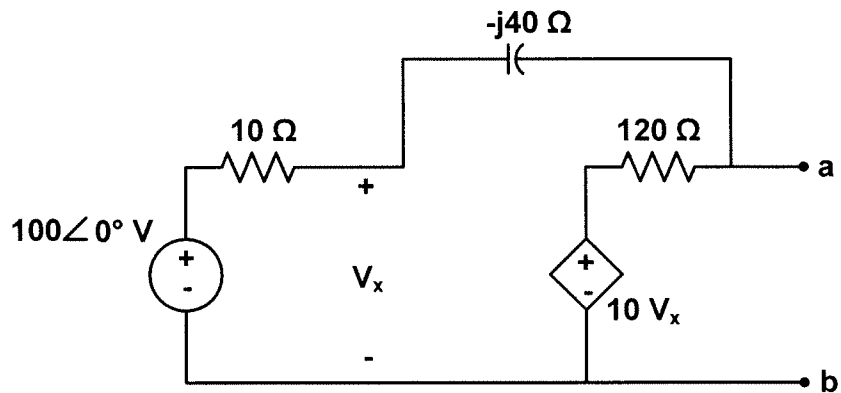2. What load should be attached to the above circuit it maximize the power delivered to the load? (4 pts)
3. Find the Thévenin equivalent of the following circuit. (8 pts)



EE281 HWK#17

1. Find V_{oc}

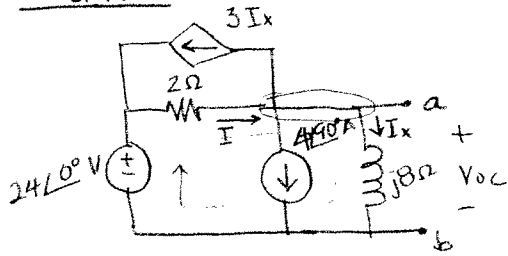

$$V_{oc} = j8I_x$$

$$\text{KVL: } -24\angle 0^\circ + 2I + j8I_x = 0$$

$$\textcircled{1} \quad 2I + j8I_x = 24$$

$$\text{KVL: } -I + 4\angle 90^\circ + I_x + 3I_x = 0$$

$$\textcircled{2} \quad -I + 4I_x = -4\angle 90^\circ = -j4$$

$$2I + j8I_x = 24$$

$$2(-I + 4I_x = -j4)$$


$$(8+j8)I_x = 24-j8$$

$$I_x = \frac{24-j8}{8+j8} = 1-j2 \text{ A}$$

$$V_{oc} = j8I_x = 16+j8 \text{ V} \\ = 17.9\angle 26.6^\circ \text{ V}$$

$$Z_{th} = \frac{V_{oc}}{I_{sc}} = \frac{16+j8}{12-j4} = 1+j1\Omega \\ = 1.41\angle 45^\circ \Omega$$


Find I_{sc}

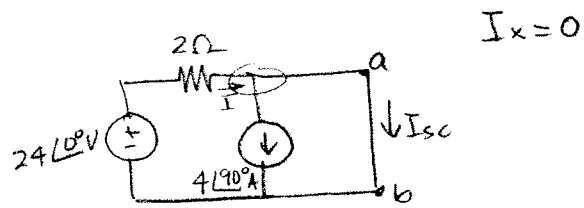

$$\text{KVL: } -24\angle 0^\circ + 2I = 0 \\ I = 12 \text{ A}$$


$$\text{KCL: } -I + 4\angle 90^\circ + I_{sc} = 0$$
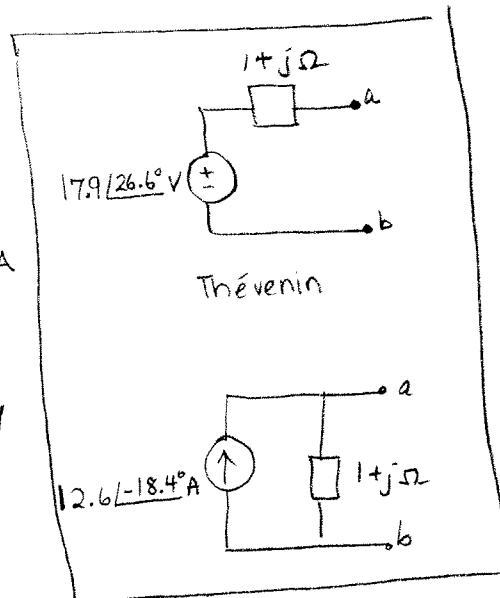
$$I_{sc} = I - 4\angle 90^\circ = 12-j4 \text{ A} \\ = 12.6\angle -18.4^\circ \text{ A}$$



$$2. \quad Z_{Load} = Z_{th}^* = 1-j\Omega$$

3. Find V_{oc}

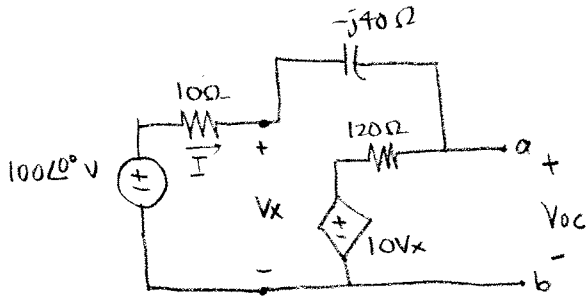

KVL: $-100\angle 0^\circ + (100 - j40)I + 10V_x = 0$

KVL: $-100\angle 0^\circ + 10I + V_x = 0$

$$\begin{aligned} (100 - j40)I + 10V_x &= 100\angle 0^\circ \\ -10(10I + V_x) &= 100\angle 0^\circ \end{aligned}$$

$$(30 - j40)I = -900$$

$$I = \frac{-900}{30 - j40} = 18\angle -126.9^\circ \text{ A}$$

$$V_x = 100 - 10I = 258\angle 34.7^\circ \text{ V}$$


KVL: $120I + 10V_x - V_{oc} = 0$

$$V_{oc} = 120I + 10V_x = 834\angle -20.1^\circ \text{ V}$$


$$= 783.2 - j286.6 \text{ V}$$

$$Z_{th} = \frac{V_{oc}}{I_{sc}} = 241.5\angle -26.6^\circ \Omega$$

$$= 215.9 - j108.2 \Omega$$

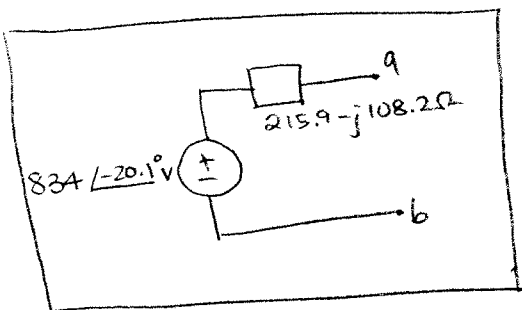

Find I_{sc}

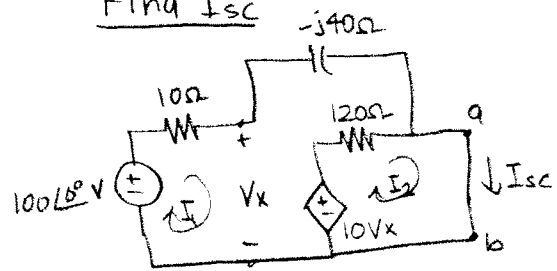

$$I_{sc} = I_2$$

m1: $-100\angle 0^\circ + (100 - j40)I_1 + 120(I_1 - I_2) + 10V_x = 0$

m2: $-10V_x + 120(I_2 - I_1) = 0$

KVL: $-100\angle 0^\circ + 10I_1 + V_x = 0$

$$V_x = 100 - 10I_1$$

(m2) $120(I_2 - I_1) - 1000 + 100I_1 = 0$

$$\begin{aligned} -20I_1 + 120I_2 &= 1000 \\ -I_1 + 6I_2 &= 50 \end{aligned}$$

(m1) $(100 - j40)I_1 + 120(I_1 - I_2) + 1000 - 100I_1 = 100$

$$\begin{aligned} (30 - j40)I_1 - 120I_2 &= -900 \\ (3 - j4)I_1 - 12I_2 &= -90 \end{aligned}$$

$$\begin{aligned} 2(-I_1 + 6I_2) &= 50 \\ (3 - j4)I_1 - 12I_2 &= -90 \end{aligned}$$


$$\begin{aligned} (1 - j4)I_1 &= 10 \\ I_1 &= \frac{10}{1 - j4} = 2.4\angle 76.0^\circ \end{aligned}$$

$$I_2 = \frac{50 + I_1}{6} = 3.45\angle 6.5^\circ$$

$$I_{sc} = 3.45\angle 6.5^\circ \text{ A}$$


$$= 3.43 + j0.39 \text{ A}$$

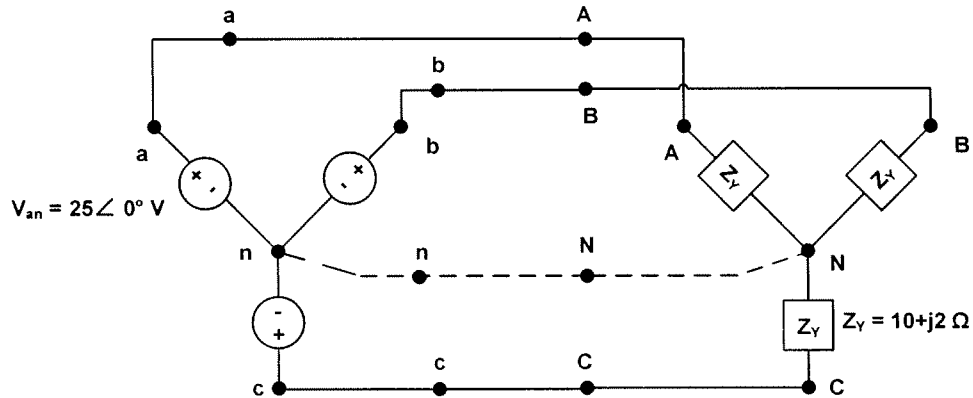- Each phase of a Y-connected load consists of a $50\text{-}\Omega$ resistance in parallel with a 200-mH inductance. Find the impedance of an equivalent Δ -connected load. Assume 60-Hz operation. (4 pts)
- For the following balanced three-phase system, assume a positive phase sequence and find:



- The line-to-neutral voltages, V_{BN} and V_{CN} , at the load. (3 pts)
- The line-to-line voltages, V_{ab} , V_{bc} , and V_{ca} . (5pts)
- The line currents, I_{aA} , I_{bB} , and I_{cC} . (5 pts)
- If, instead, the system had a negative phase sequence, find V_{BN} and V_{CN} . (3pts)

EE281 Homework #18

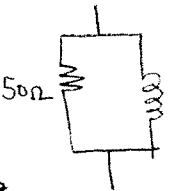1. Z_Y :  200mH
 $f = 60\text{-Hz}$
 $\omega = 2\pi f = 120\pi \text{ rad/sec.}$
 $j(120\pi)(0.2) = j75.4\Omega$

$$Z_Y = 50 \parallel j75.4 = \frac{50(j75.4)}{50 + j75.4}$$

$$= 41.67 \angle 33.5^\circ \Omega$$

$$= 34.7 + j23.0\Omega$$

$$Z_\Delta = 3Z_Y$$

$$= 125.01 \angle 33.5^\circ \Omega$$

$$= 104.2 + j69.1\Omega$$

2. a) $V_{BN} = 25 \angle -120^\circ \text{ V}$
 $V_{CN} = 25 \angle -240^\circ \text{ V}$

b) $V_{ab} = V_{an} (\sqrt{3} \angle 30^\circ)$
 $= (25 \angle 0^\circ) (\sqrt{3} \angle 30^\circ)$

$$V_{ab} = 25\sqrt{3} \angle 30^\circ \text{ V}$$

$$V_{bc} = 25\sqrt{3} \angle -90^\circ \text{ V}$$

$$V_{ca} = 25\sqrt{3} \angle -210^\circ \text{ V}$$

c) $I_{aA} = \frac{V_{AN}}{Z_Y} = \frac{25 \angle 0^\circ \text{ V}}{41.67 \angle 33.5^\circ \Omega}$

$$I_{aA} = 0.6 \angle -33.5^\circ \text{ A}$$


$$I_{bB} = 0.6 \angle -153.5^\circ \text{ A}$$

$$I_{cC} = 0.6 \angle -273.5^\circ \text{ A}$$


d) $V_{BN} = 25 \angle 120^\circ \text{ V}$
 $V_{CN} = 25 \angle 240^\circ \text{ V}$

equivalent angles
are acceptable.

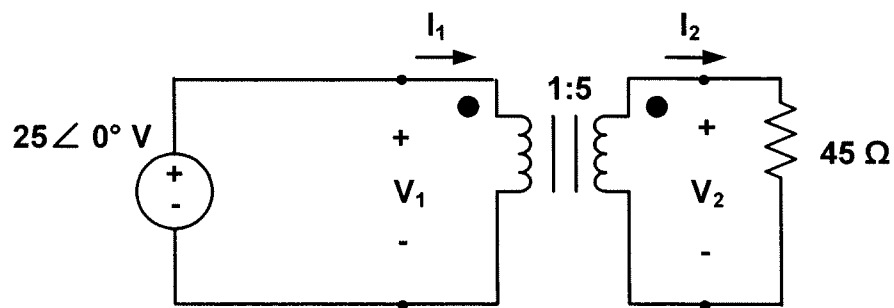1. Find the turns ratio in an ideal transformer necessary to step up a $120\text{-V}_{\text{rms}}$ voltage to $5000\text{ V}_{\text{rms}}$. (3 pts)
2. Find the turns ratio in an ideal transformer necessary to step down a 20-A_{rms} current to $2.5\text{ A}_{\text{rms}}$. (3 pts)
3. Find the phasors V_1 , V_2 , I_1 , I_2 , and the average power delivered to the $45\text{-}\Omega$ load. (8 pts)



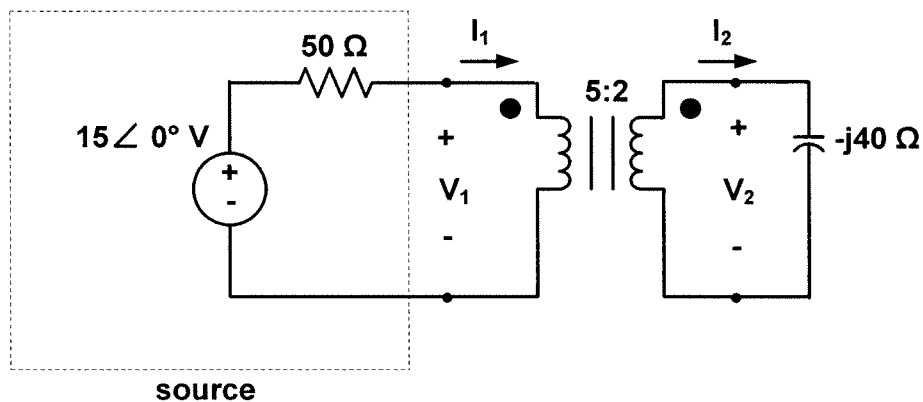4. Use impedance transformations (reflected impedances) to find the impedance seen by the source in the following circuit. (6 pts)



EE281 Homework #19

1. $V_2 = \frac{N_2}{N_1} V_1$

$$5000 = \frac{N_2}{N_1} (120)$$

$$\frac{N_2}{N_1} = \frac{5000}{120} = \frac{250}{6} = \frac{125}{3}$$


$$N_1 : N_2 = 3 : 125$$

2. $I_2 = \frac{N_1}{N_2} I_1$

$$2.5 = \frac{N_1}{N_2} (20)$$

$$\frac{N_1}{N_2} = \frac{2.5}{20} = \frac{25}{200} = \frac{1}{8}$$

$$N_1 : N_2 = 1 : 8$$

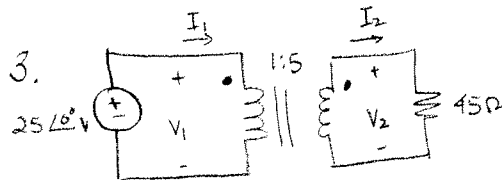

$$V_1 = 25 \angle 0^\circ \text{ V}$$

$$V_2 = \left(\frac{5}{1}\right) (25 \angle 0^\circ)$$

$$V_2 = 125 \angle 0^\circ \text{ V}$$

$$I_2 = \frac{V_2}{45 \Omega} = \frac{125 \angle 0^\circ}{45}$$

$$I_2 = 2.78 \angle 0^\circ \text{ A}$$

$$I_1 = \frac{N_2}{N_1} I_2 = \left(\frac{5}{1}\right) 2.78 \angle 0^\circ$$

$$I_1 = 13.89 \angle 0^\circ \text{ A}$$


4. $Z'_L = \left(\frac{N_1}{N_2}\right)^2 Z_L$

$$= \left(\frac{5}{2}\right)^2 (-j40)$$


$$Z'_L = -j250 \Omega$$

$$= 250 \angle -90^\circ \Omega$$

1. For the following lowpass filter:

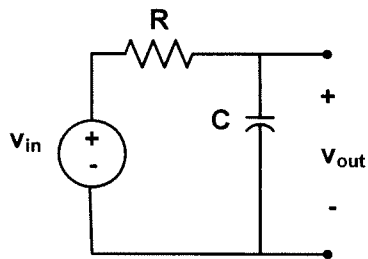


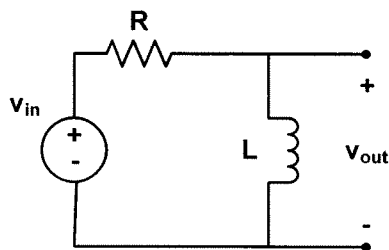- Find the transfer function $H(j\omega)$, in terms of ω , R , and C . (3 pts)
 - If $R=100\ \Omega$, find the value of C needed for a $\frac{1}{2}$ -power frequency of 5000 rad/sec. (3 pts)
 - If $v_{in} = 20\cos(500t) + 20\cos(8000t)$ V, find $v_{out}(t)$ for the values of R and C from the previous part. (5 pts)
2. For the following filter, determine:



- The transfer function $H(j\omega)$, in terms of ω , R , and L . (4 pts)
- The $\frac{1}{2}$ -power frequency (in rad/sec) if $R=1000\ \Omega$ and $L=0.1$ mH. (3 pts)
- Is this a lowpass or highpass filter? (2 pts)

Homework #20

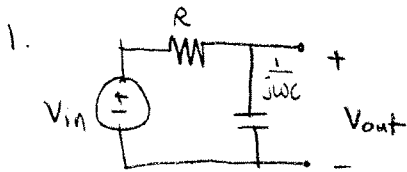

$$a) H(j\omega) = \frac{1/j\omega C}{R + 1/j\omega C} = \boxed{\frac{1}{1 + j\omega RC}}$$

$$b) \frac{1}{2} \text{ power freq} = \frac{1}{RC}$$
$$5000 = \frac{1}{100 C}$$
$$\boxed{C = 2 \mu F}$$

$$c) V_{in} = 20 \cos(500t) + 20 \cos(8000t)$$

$$\omega = 500$$

$$V_{out} = H(j500) 20 \angle 0^\circ$$

$$= \frac{1}{1 + j(500)(100)(2 \times 10^{-6})} 20 \angle 0^\circ = 19.9 \angle -5.71^\circ$$

$$V_{out} = 19.9 \cos(500t - 5.71^\circ)$$

$$\omega = 8000$$


$$V_{out} = H(j8000) 20 \angle 0^\circ$$

$$= \frac{1}{1 + j(8000)(100)(2 \times 10^{-6})} 20 \angle 0^\circ = 10.60 \angle -58.0^\circ$$

$$V_{out} = 10.60 \cos(8000t - 58.0^\circ)$$

$$\boxed{V_{out}(t) = 19.9 \cos(500t - 5.71^\circ) + 10.60 \cos(8000t - 58.0^\circ) \text{ V}}$$

2.

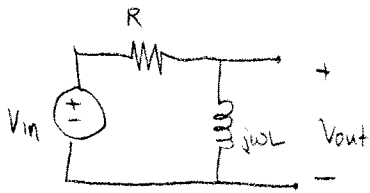

$$a) \quad H(j\omega) = \frac{j\omega L}{R + j\omega L}$$

$$b) \quad \omega = \frac{R}{L} = \frac{1000}{0.1 \times 10^{-3}} = 1 \times 10^7 \text{ rad/sec}$$


$$c) \quad |H(j\omega)| = \frac{\omega L}{\sqrt{R^2 + (\omega L)^2}}$$

$$|H(j0)| = 0$$


$$|H(j\infty)| = 1$$

high pass

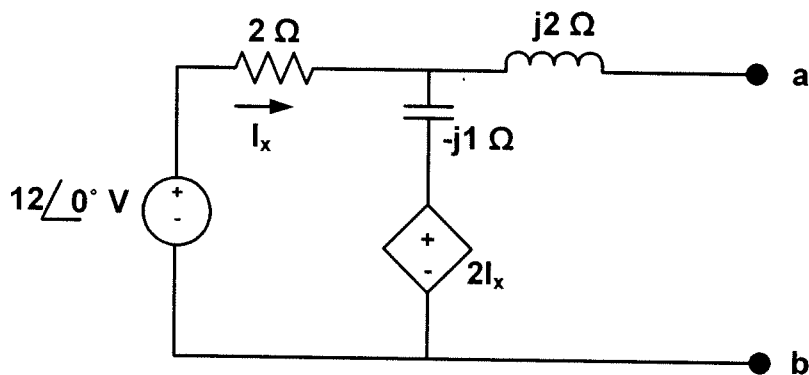7. Find the Thévenin equivalent of the following circuit.



(20 pts)

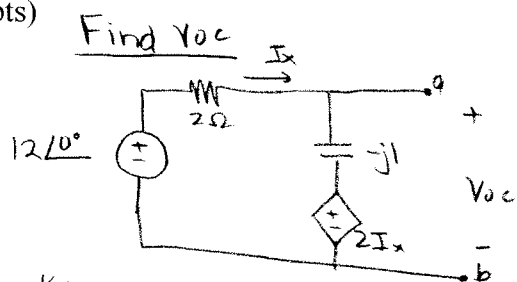


KVL:

$$-12 + 2I_x - jI_x + 2I_x = 0$$

$$(4-j)I_x = 12$$

$$I_x = 12 / (4-j) = 2.91 \angle 14.04^\circ$$
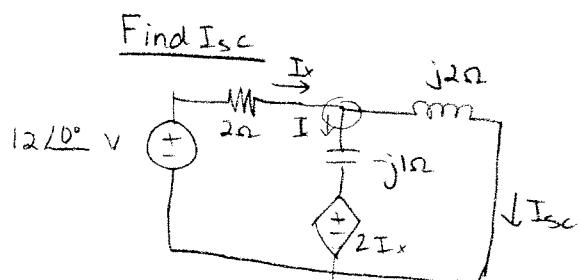
$$V_{oc} = -jI_x + 2I_x = (2-j)I_x = 6.51 \angle -12.53^\circ \text{ V}$$



KVL outer loop: $-12 + 2I_x + j2I_{sc} = 0$

① $2I_x + j2I_{sc} = 12 \Rightarrow I_x = \frac{12 - j2I_{sc}}{2} = 6 - jI_{sc}$

KCL: $I = I_x - I_{sc}$

KVL left loop: $-12 + 2I_x - jI + 2I_x = 0$


$$-12 + 4I_x - j(I_x - I_{sc}) = 0$$

② $(4-j)I_x + jI_{sc} = 12$

$$= 1.53 \angle 85.6^\circ \Omega \quad (4-j)(6 - jI_{sc}) + jI_{sc} = 12$$

$$= 0.12 + j1.53 \Omega \quad (-j(4-j) + j)I_{sc} = 12 - 6(4-j)$$
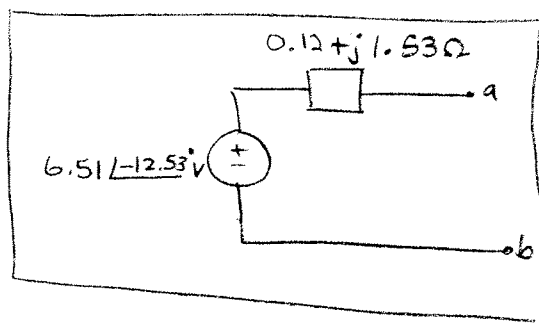
$$I_{sc} = \frac{12 - 6(4-j)}{-j(4-j) + j} = -0.6 - j4.2 = 4.24 \angle -98.13^\circ \text{ A}$$




Exam Practice

Final Exam Review (DM)

— Things to know — Final Exam (not on crib sheet)

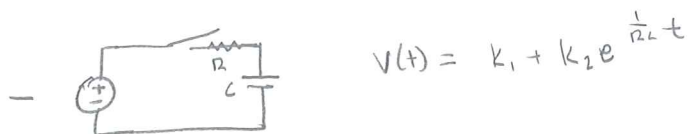— P. Factor = $\cos(\theta)$ where θ is angle of impedance, $\mathbf{Z}$



Leading = θ is negative

Lagging =

— $I_{rms} = \frac{V_{rms}}{|\mathbf{Z}|}$ So if $V_s = 20 \angle 60^\circ$ & $\mathbf{Z} = 50 \angle 45^\circ$, $I_{rms} = \frac{20}{50}$

— units of Q, apparent power, are VA

— $\mathbf{Z}_L = j\omega L$

— $\mathbf{Z}_C = \frac{1}{j\omega C}$

— phasor voltage written in terms of cosine $6(\sin(t+5)) = 6\cos(t-85)$
 $= 6 \angle -85^\circ$


natural solution = homogeneous soln so $Ai + B\frac{di}{dt} = 0$

particular solution = only right side of eqn so $f(\sin, \cos) = -A\cos(4t) + b\sin(4t)$
• same form as source takes

— underdamped — real & imaginary

— overdamped — real only

— critically — imaginary only

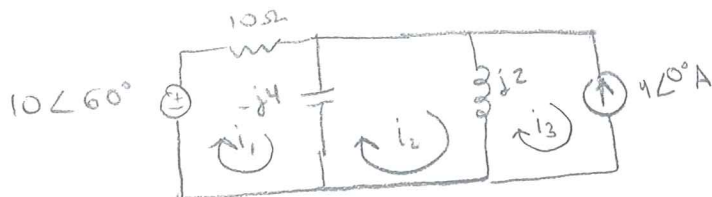

Set up mesh eq's for I_1, I_2, I_3


$$10\angle 60^\circ - 10 I_1 + j4(I_1 - I_2) = 0$$

$$j4(i_2 - i_1) - j2(i_2 - i_3) = 0$$

$$-j2(i_3 - i_2) = 0$$

$$i_3 = -4\angle 0^\circ \text{ A}$$
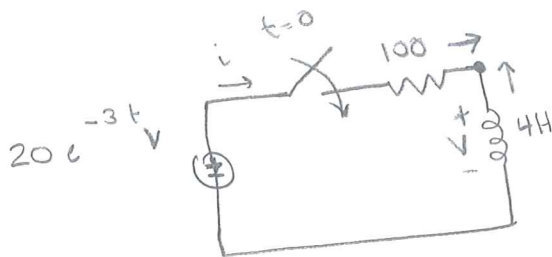
$$\begin{bmatrix} -10+j4 & -j4 & 0 \\ -j4 & j2 & j2 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \end{bmatrix} = \begin{bmatrix} 10\angle 60^\circ \\ 0 \\ -4\angle 0^\circ \end{bmatrix}$$



$i =$

$$\text{KVL} \quad 20e^{-3t} - 100i - 4 \frac{di}{dt} = 0$$

$$\frac{di}{dt} + 25i = 5e^{-3t}$$

$\uparrow$
 $i_p(t)$

$$sV(s) + 25V(s) = 0$$



$$V(s)(s+25) = 0 \Rightarrow i_1(t) = k_1 e^{-25t}$$

$$i_p(0) = e^{-3t}$$

Sample Problems – Exam 4

EE281

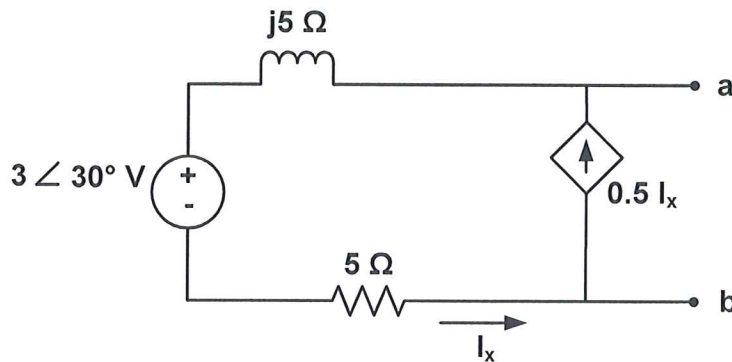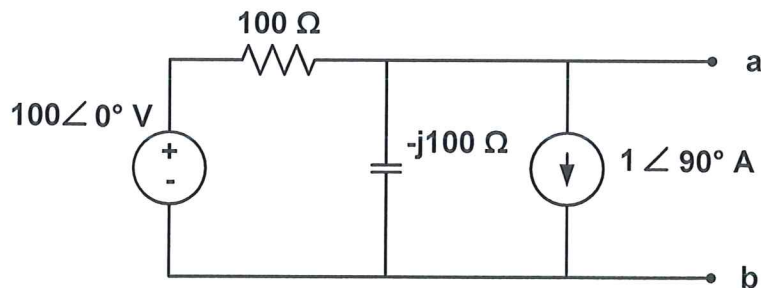1. Find the Thevenin equivalents for each of the following circuits.



2. What load impedance should be placed between the terminals in each of the previous circuits to that maximum power is delivered to the load?

$$P_{max}, Z = Z_{th}^*$$

3. A Δ -connected load has an impedance $Z_{\Delta} = 5 - j2 \Omega$. What is the equivalent Y-connected load?

4. A balanced positive-phase sequence, Y-connected, 60-Hz, three-phase source has a line-to-line voltage of $440 V_{rms}$. It is connected to a balanced three-phase, Y-connected load with an impedance $Z_Y = 5 - j2 \Omega$. Assume V_{an} has a zero phase. Find the line-to-neutral voltage phasors, line-to-line voltage phasors, line current phasors, and the average and reactive power delivered to the load.


$$V_{an} = \underline{\quad\quad\quad} \angle 0^\circ$$

$$\begin{aligned} V_{ab} \\ V_{bc} \\ V_{ca} \end{aligned}$$

$$\begin{aligned} V_{an} \\ V_{bn} \\ V_{cn} \end{aligned}$$


5. Find the turns ratio necessary to step down a $440\text{-V}_{\text{rms}}$ AC source to 20 V_{rms} . Assume the transformer is ideal.

6. For the circuit below, find:

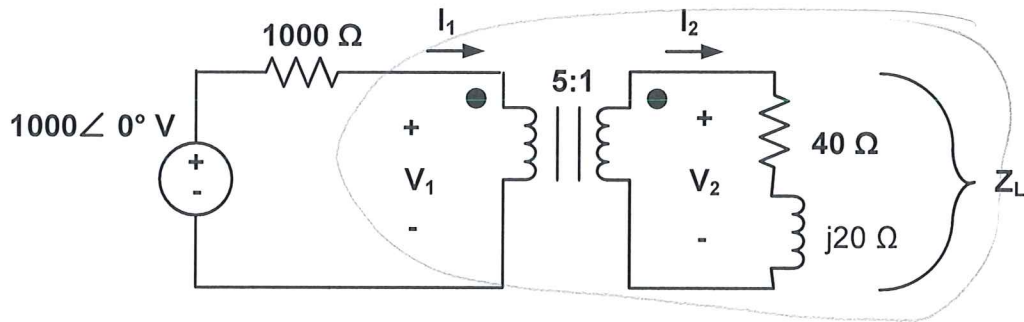

- The total impedance seen by the 1000-V source.
- The average power delivered to the load Z_L .
- The phasors V_1 , V_2 , I_1 , and I_2 .


7. For the following filter, find:

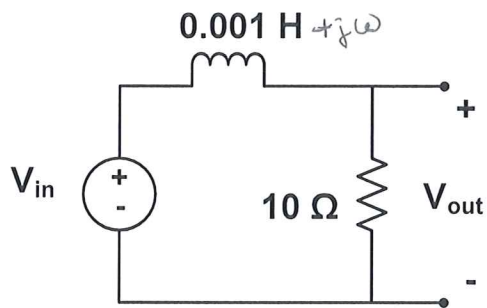



- The transfer function $H(j\omega) = \frac{V_{\text{out}}}{V_{\text{in}}}$.
- The half-power frequency in rad/sec.
- $v_{\text{out}}(t)$ if $v_{\text{in}}(t) = 50 \cos(100t) + 50 \cos(5000t - 45^\circ)\text{ V}$.

EE281 Sample Problems - Exam 4


(1a)

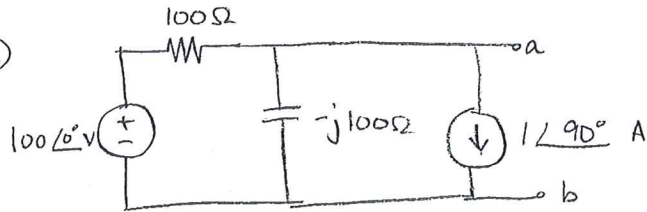

Using source transformations

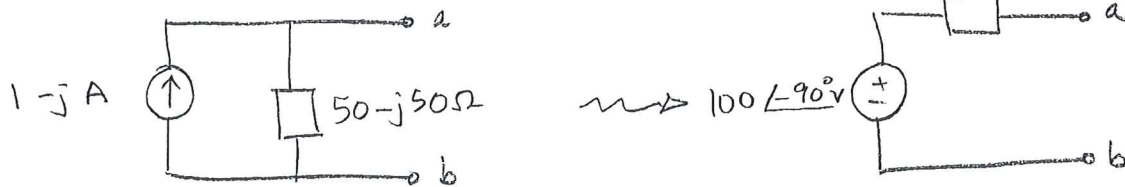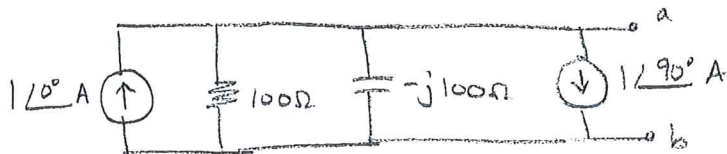


(1b)

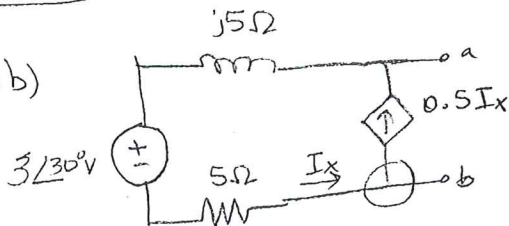

Find V_{oc}

KCL: $I_x = 0.5I_x \Rightarrow I_x = 0$
 Thus no voltage drop across 5-Ω resistor or inductor.
 $V_{oc} = 3\angle30^\circ \text{ V}$

Find I_{sc}

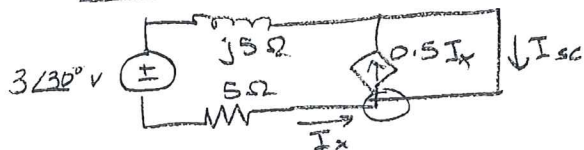


$$\begin{aligned} \text{KCL: } I_x + I_{sc} - 0.5I_x &= 0 \\ 0.5I_x + I_{sc} &= 0 \end{aligned}$$

$$\begin{aligned} \text{KVL: } +3\angle30^\circ + 5I_x + j5I_x &= 0 \\ (5+j5)I_x &= -3\angle30^\circ \\ I_x &= 0.424\angle165^\circ \end{aligned}$$

$$I_{sc} = -0.5I_x = 0.212\angle-15^\circ \text{ A}$$
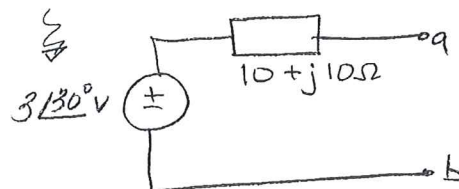
$$\begin{aligned} Z_{th} &= V_{oc} / I_{sc} = \frac{3\angle30^\circ}{0.212\angle-15^\circ} = 14.14\angle45^\circ \Omega \\ &= 10 + j10\Omega \end{aligned}$$



$$(2a) \quad Z_L = Z_S^* = 50 + j50 \Omega$$

$$(2b) \quad Z_L = Z_S^* = 10 - j10 \Omega$$

$$(3) \quad Z_Y = \frac{Z_\Delta}{3} = \frac{5-j2}{3} = \frac{5}{3} - j\frac{2}{3} \Omega$$

$$(4) \quad V_{ab} = V_{an} (\sqrt{3} \angle 30^\circ)$$

$$V_{an} = \frac{V_{ab}}{\sqrt{3} \angle 30^\circ} = \frac{440 \angle 30^\circ}{\sqrt{3} \angle 30^\circ} = 254.03 \angle 0^\circ \text{ V}$$

$$V_{an} = V_{AN} = 254.03 \angle 0^\circ \text{ V}$$

$$V_{bn} = V_{BN} = 254.03 \angle -120^\circ \text{ V}$$

$$V_{cn} = V_{CN} = 254.03 \angle -240^\circ \text{ V}$$

$$V_{ab} = V_{AB} = 440 \angle 30^\circ \text{ V}$$

$$V_{bc} = V_{BC} = 440 \angle -90^\circ \text{ V}$$

$$V_{ca} = V_{CA} = 440 \angle 150^\circ \text{ V}$$

$$I_{aA} = \frac{V_{AN}}{Z_Y} = \frac{254.03 \angle 0^\circ}{5-j2} = 47.17 \angle 21.8^\circ \text{ A}$$

$$I_{bB} = 47.17 \angle -98.2^\circ \text{ A}$$

$$I_{cC} = 47.17 \angle 141.8^\circ \text{ A}$$

$$P = 3 V_{Y_{rms}} I_{L_{rms}} \cos \theta = 3 (254.03) (47.17) \cos (-21.8^\circ) = 33377 \text{ W}$$

$$Q = 3 V_{Y_{rms}} I_{L_{rms}} \sin \theta = 3 (254.03) (47.17) \sin (-21.8^\circ) = -13350 \text{ VAR}$$

$$(5) \quad V_1 = \frac{N_1}{N_2} V_2$$

$$440 = \frac{N_1}{N_2} (20)$$

$$\frac{N_1}{N_2} = 22$$


$$N_1 : N_2 = 22 : 1$$

$$(6a) \quad Z_L = 40 + j20$$

$$Z_L' = \left(\frac{N_1}{N_2}\right)^2 Z_L = \left(\frac{5}{1}\right)^2 (40 + j20) = 1000 + j500 \Omega$$

$$Z_L'' = 1000 + Z_L' = 2000 + j500 \Omega$$
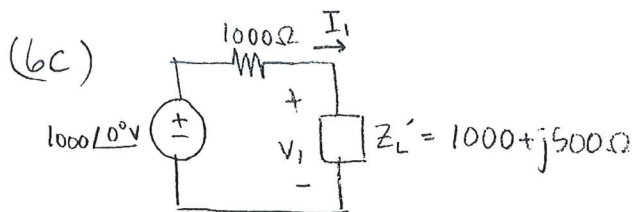
$$(6b) \quad P = I_{2_{rms}}^2 R = \left(\frac{2.43}{\sqrt{2}}\right)^2 (40) = 118.1 \text{ W}$$



$$V_1 = \frac{1000 + j500}{2000 + j500} (1000 \angle 0^\circ) = 542.3 \angle 12.5^\circ \text{ V}$$

$$I_1 = \frac{V_1}{Z_L'} = \frac{542.3 \angle 12.5^\circ}{1000 + j500} = 0.49 \angle -14.0^\circ \text{ A}$$

$$I_2 = \frac{N_1}{N_2} I_1 = \frac{5}{1} (0.49 \angle -14.0^\circ) = 2.43 \angle -14.0^\circ \text{ A}$$

$$V_2 = \frac{N_2}{N_1} V_1 = \frac{1}{5} (542.3 \angle 12.5^\circ) = 108.46 \angle 12.5^\circ \text{ V}$$

$$(7a) \quad V_{out} = \frac{10}{10 + j\omega(0.001)} V_{in}$$

$$H(j\omega) = \frac{10}{10 + j0.001\omega}$$

$$(7b) \quad |H(j\omega)| = \frac{10}{\sqrt{100 + (0.001\omega)^2}} = \frac{1}{\sqrt{2}}$$

$$200 = 100 + (0.001)^2 \omega^2$$

$$\omega = 10,000 \text{ rad/sec.}$$



$$(7c) \quad \begin{aligned} \omega = 100 \\ V_{in1} = 50 \angle 0^\circ \\ V_{out1} = 50 \angle 0^\circ \left(\frac{10}{10 + j0.001(100)} \right) = 49.998 \angle -0.57^\circ \end{aligned}$$

$$\begin{aligned} \omega = 5000 \\ V_{in2} = 50 \angle -45^\circ \\ V_{out2} = 50 \angle -45^\circ \left(\frac{10}{10 + j0.001(5000)} \right) = 44.721 \angle -71.57^\circ \end{aligned}$$


$$v_{out}(t) = 49.998 \cos(100t - 0.57^\circ) + 44.721 \cos(5000t - 71.57^\circ) \text{ V}$$

Exam 3 Extra Probs & Solns

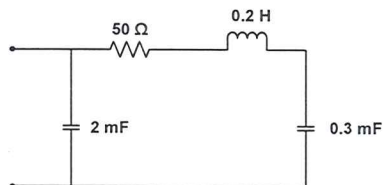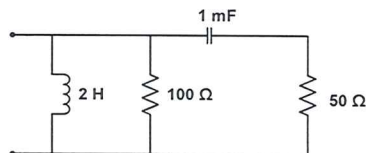6. Write each of the following as a single impedance. Assume that $\omega=100$ rad/sec.



7. In the following circuit:

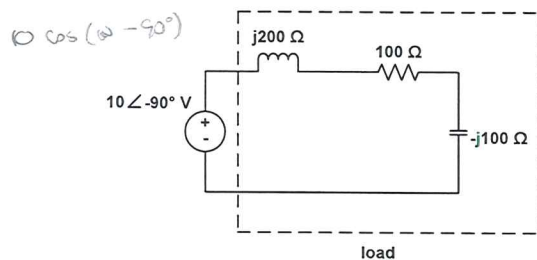

$$V_R =$$

$$(100 + j100) \Omega$$

- Calculate the average power, reactive power, and apparent power absorbed by the load.
- Draw the power triangle.
- What is the power factor?


$$P = I_{rms}^2 R = \frac{V_{rms}^2}{R} = \frac{10^2}{\sqrt{2}^2} = \frac{100}{2} = 50$$

$$PF = \cos \theta$$


EE281 – Exam 3 – Sample Problems

$$I = I \frac{\frac{1}{R_x}}{\frac{1}{R_{total}}}$$

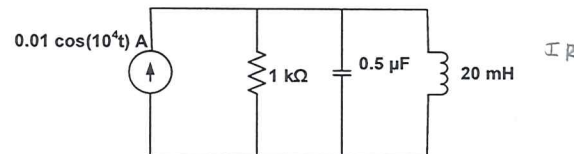
1. Redraw the following circuit in the frequency domain.



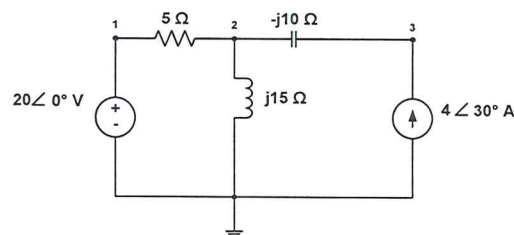- Find the steady-state current through each of the components (resistor, inductor, and capacitor) in the circuit in problem 1.
- Find the steady-state voltage across each of the components (resistor, inductor, and capacitor) in the circuit in problem 1.
- Set up the node voltage equations in matrix form to find the phasor node voltages V_1 , V_2 , and V_3 . Do not solve.



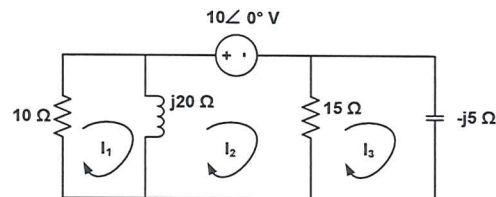5. Set up the mesh current equations in matrix form to find the phasor mesh currents I_1 , I_2 , and I_3 . Do not solve.




12. Find the RMS value of each of the following voltages.

a. $v(t) = 10 \cos(2\pi t - 40^\circ) \text{ V}$

b.


$v \text{ (volts)}$

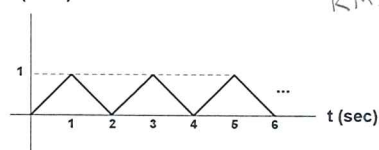


$$RMS = \sqrt{\frac{1}{T} \int_0^T f^2 dx}$$

c.

$v \text{ (volts)}$

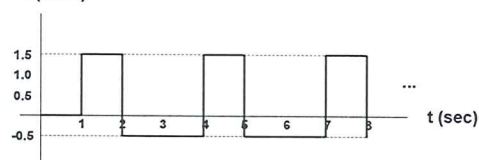


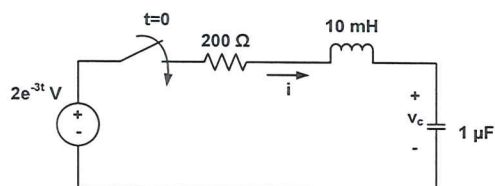13. Assuming that $v_c(0)=0$, find following for the circuit below:




- The form of the source-free (natural) solution of $i(t)$.
- The steady-state (particular) solution of $i(t)$.
- The form of the complete solution. You do not have to solve for the constants from the source-free portion.
- Is this circuit overdamped, underdamped, or critically damped?

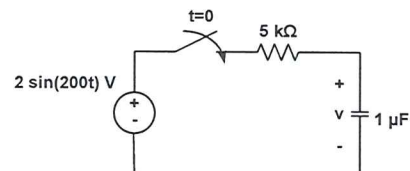
8. Find the steady-state voltage, $v(t)$, in the following circuit.



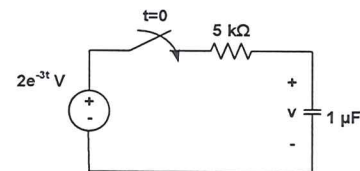9. Find the steady-state voltage (the particular response of the differential equation), $v(t)$, in the following circuit.




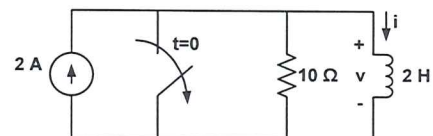
10. Assuming that the switch has been closed for a long time prior to $t=0$, find an expression for $i(t)$ and $v(t)$ in the following circuit.



11. Write the following as phasors:

- $20 \cos(2\pi t - 30^\circ)$
- $10 \sin(20t + 8^\circ)$

Volts across
component, real or img

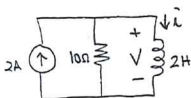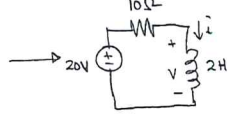10.  $\rightarrow$ 

$$-20 + 10i + 2 \frac{di}{dt} = 0$$

$$\frac{di}{dt} + 5i = 10$$

$$\frac{di}{dt} + 5i = 0$$

$$\lambda + 5 = 0$$

$$\lambda = -5$$

$$i_h(t) = K_1 e^{-5t}$$

$$i_p(t) = K_2$$

$$0 + 5K_2 = 10$$

$$K_2 = 2$$

$$i_p(t) = 2$$

$$i(t) = K_1 e^{-5t} + 2$$

$$i(0) = 0 = K_1 + 2 \rightarrow K_1 = -2$$

$$i(t) = 2 - 2e^{-5t} \text{ A}$$

$$v(t) = L \frac{di}{dt} = 2(10e^{-5t})$$

$$v(t) = 20e^{-5t} \text{ V}$$

11. a) $20 \angle -30^\circ$
b) $10 \angle -82^\circ$

12. a) $\frac{10}{\sqrt{2}} \text{ V}$


b) $V_{rms} = \sqrt{\frac{1}{2} \left[\int_0^1 t^2 dt + \int_1^2 (2-t)^2 dt \right]} = \sqrt{\frac{1}{2} \left[\frac{t^3}{3} \Big|_0^1 + \frac{(2-t)^3}{-3} \Big|_1^2 \right]}$

$$= \sqrt{\frac{1}{2} \left[\left(\frac{1}{3} \right) + \left(\frac{1}{3} \right) \right]} = \frac{1}{\sqrt{3}} \text{ V}$$

c) $V_{rms} = \sqrt{\frac{1}{3} \left[\int_1^2 (1.5)^2 dt + \int_2^4 (-0.5)^2 dt \right]}$

$$= \sqrt{\frac{1}{3} \left[2.25t \Big|_1^2 + 0.25t \Big|_2^4 \right]} = \sqrt{\frac{1}{3} [2.25 + 0.25(2)]}$$

$$= 0.957 \text{ V}$$

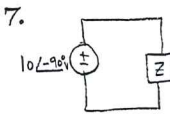7. 

$$V_{rms} = \frac{10}{\sqrt{2}} \text{ V}$$

$$Z = 100 \angle j100^\circ = 141.4 \angle 45^\circ \Omega$$

$$V_R = \frac{100}{100 + j100} 10 \angle -90^\circ = 7.07 \angle -135^\circ \text{ V}$$

$$V_L = \frac{j100}{100 + j100} 10 \angle -90^\circ = 7.07 \angle -45^\circ \text{ V}$$


a) $P = \frac{V_{rms}^2}{R} = \frac{(7.07 \angle -45^\circ)^2}{100} = 0.25 \text{ W}$

$$Q = \frac{V_{rms}^2}{X} = \frac{(7.07 \angle -45^\circ)^2}{100} = 0.25 \text{ VAR}$$


$$\text{app power} = \sqrt{P^2 + Q^2} = 0.35 \text{ VA}$$

$$P = I_{rms}^2 R$$

$$Q = I_{rms}^2 X$$

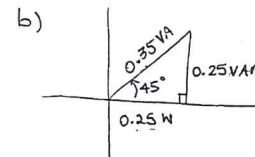

c) $PF = \cos 45^\circ = \frac{1}{\sqrt{2}} = 0.707$

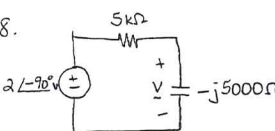8. 

$$V = \frac{-j5000}{5000 - j5000} 2 \angle -90^\circ = 1.414 \angle -135^\circ \text{ V}$$

$$v(t) = 1.414 \cos(200t - 135^\circ) \text{ V}$$

9. $(1 \times 10^{-6}) \frac{dv}{dt} + \frac{v - 2e^{-3t}}{5000} = 0$

$$\frac{dv}{dt} + 200v = 400e^{-3t}$$


$$v_p(t) = Ae^{-3t}$$

$$-3Ae^{-3t} + 200Ae^{-3t} = 400e^{-3t}$$

$$197A = 400$$

$$A = 2.03 = 400/197$$
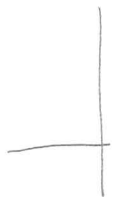
$$v_p(t) = \frac{400}{197} e^{-3t} \text{ V}$$



$$P = I_{rms}^2 R$$

$$Q = I_{rms}^2 X$$

$$v(t) = 20 \cos(15t + 30^\circ)$$


$$V_{rms} = 20 \angle 30^\circ$$

5. mesh 1
 $10I_1 + j20(I_1 - I_2) = 0$
 $(10 + j20)I_1 - j20I_2 = 0$


mesh 3
 $-j5I_3 + 15(I_3 - I_2) = 0$
 $-15I_2 + (15 - j5)I_3 = 0$

mesh 2
 $j20(I_2 - I_1) + 10\angle 0^\circ + 15(I_2 - I_3) = 0$
 $-j20I_1 + (15 + j20)I_2 - 15I_3 = -10\angle 0^\circ$
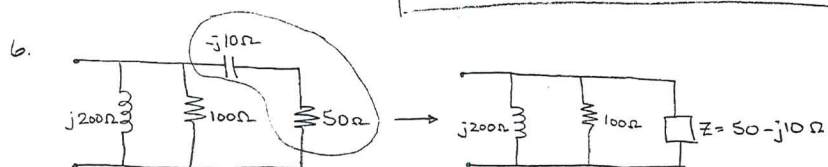
$$\begin{bmatrix} 10+j20 & -j20 & 0 \\ -j20 & 15+j20 & -15 \\ 0 & -15 & 15-j5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 0 \\ -10\angle 0^\circ \\ 0 \end{bmatrix}$$



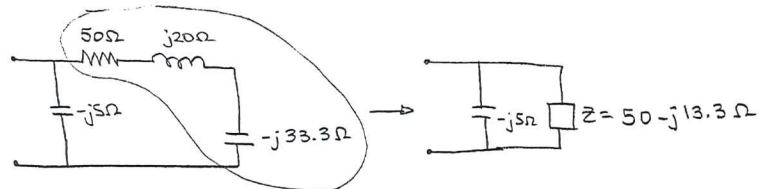
$$Z = \frac{1}{\frac{1}{j200} + \frac{1}{100} + \frac{1}{50-j10}} = 34.18 \angle -2.26^\circ \Omega = 34.16 + j1.35 \Omega$$



$$Z = \frac{(-j5)(50 - j13.3)}{-j5 + 50 - j13.3} = 0.44 - j4.84 \Omega = 4.86 \angle -84.8^\circ \Omega$$

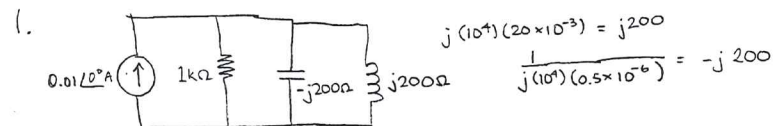EE281 - Exam 3 Sample Problems - solutions



2. $I_R = \frac{\frac{1}{1000}}{\frac{1}{1000} + \frac{1}{-j200} + \frac{1}{j200}} (0.01 \angle 0^\circ) = 0.01 \angle 0^\circ \text{ A}$

$$i_R(t) = 0.01 \cos(10^4 t) \text{ A}$$

$$I_C = \frac{1/j200}{\frac{1}{1000} + \frac{1}{-j200} + \frac{1}{j200}} (0.01 \angle 0^\circ) = 0.05 \angle 90^\circ \text{ A}$$

$$i_C(t) = 0.05 \cos(10^4 t + 90^\circ) \text{ A}$$

$$I_L = \frac{1/j200}{\frac{1}{1000} + \frac{1}{-j200} + \frac{1}{j200}} (0.01 \angle 0^\circ) = 0.05 \angle -90^\circ \text{ A}$$

$$i_L(t) = 0.05 \cos(10^4 t - 90^\circ) \text{ A}$$

3. $V_R = I_R Z_R = (0.01 \angle 0^\circ)(1000) = 10 \angle 0^\circ \text{ V}$

$$v_R(t) = v_C(t) = v_L(t) = 10 \cos(10^4 t) \text{ V}$$

4. node 1

$$V_1 = 20 \angle 0^\circ$$

node 2

$$\frac{V_2 - V_1}{5} + \frac{V_2}{j15} + \frac{V_2 - V_3}{-j10} = 0$$

$$-\frac{1}{5}V_1 + (\frac{1}{5} + \frac{j}{30})V_2 - \frac{1}{10}jV_3 = 0$$

node 3

$$\frac{V_3 - V_2}{-j10} - 4 \angle 30^\circ = 0$$

$$\begin{bmatrix} 1 & 0 & 0 \\ -\frac{1}{5} & \frac{1}{5} + \frac{j}{30} & -\frac{j}{10} \\ 0 & -\frac{j}{10} & \frac{1}{10} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix} = \begin{bmatrix} 20 \angle 0^\circ \\ 0 \\ 4 \angle 30^\circ \end{bmatrix}$$

$$13. a) -2e^{-3t} + 200\dot{i} + (10 \times 10^{-3}) \frac{di}{dt} + \frac{1}{1 \times 10^{-6}} \int_{-\infty}^t \dot{i} d\lambda = 0$$

$$\frac{d^2 i}{dt^2} + 20,000 \frac{di}{dt} + (1 \times 10^8) i = -600 e^{-3t}$$

$$\frac{d^2 i}{dt^2} + (2 \times 10^4) \frac{di}{dt} + (1 \times 10^8) i = 0$$

$$\lambda^2 + (2 \times 10^4) \lambda + (1 \times 10^8) = 0$$

$$\lambda = \frac{-(2 \times 10^4) \pm \sqrt{(2 \times 10^4)^2 - 4(1 \times 10^8)}}{2} = -10,000 \pm 10,000$$

$$i_h(t) = K_1 e^{-10,000t} + K_2 t e^{-10,000t}$$

$$b) i_p(t) = A e^{-3t}$$

$$9A e^{-3t} + 20000(-3A e^{-3t}) + (1 \times 10^8) A e^{-3t} = -600 e^{-3t}$$

$$9A - 60,000A + (1 \times 10^8)A = -600$$

$$(9940009)A = -600 \Rightarrow A = 6.004 \times 10^{-6}$$

$$i_p(t) = (6.004 \times 10^{-6}) e^{-3t} A$$

$$c) i(t) = K_1 e^{-10,000t} + K_2 t e^{-10,000t} + (6.004 \times 10^{-6}) e^{-3t} A$$

d) critically damped

Exam 3

P.F. = ?

1) a) P.F. = $\cos(7.12)$, = .992, lagging

b) RMS current

$$I_{rms} = \frac{V_{rms}}{|Z|} = \frac{20 \angle 60^\circ}{(20 \angle 67.13)} = \boxed{.9992} \angle -7.13^\circ \text{ A}_{rms}$$

c) $P_{real} = \frac{1}{2} V_m I_m \cos \theta$

$$= \frac{1}{2} (20)(.9992) \cos(7.13) = \boxed{1.96 \text{ W}}$$

d) $P_{apparent} = Q = \frac{1}{2} (20)(.9992) \sin(7.13) = \boxed{0.123 \text{ VA}}$

2) equivalent impedance $2 \angle -90$


OK ✓

3) $V(t) = 6 \sin(14t + 5^\circ) \text{ V}$

find RMS of $V(t)$ $= 6 \times \frac{1}{\sqrt{2}}$ OK ✓

phasor

$6 \angle 5^\circ$

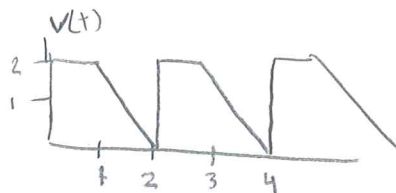find V_{rms} 

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T V^2 dt}$$

$$= \sqrt{\frac{1}{2} \int_0^1 2^2 dt + \frac{1}{2} \int_1^2 (4-2t)^2 dt}$$


$$4 + \int_1^2 (16 - 4t + 4t^2) dt$$

$$4 + 4 \int_1^2 (4 - t + t^2) dt = \sqrt{4 + 4 \left[4t - \frac{t^2}{2} + \frac{t^3}{3} \right]_1^2}$$

$$= \sqrt{4 + 4 \left[8 - 4 - \frac{4}{2} + \frac{1}{2} + \frac{8}{3} - \frac{1}{3} \right]} = 4.83$$

1) $\left(\frac{1}{8} + \frac{1}{40}\right)^{-1}$ 6.67Ω $\checkmark$ OK


2) Simplify:

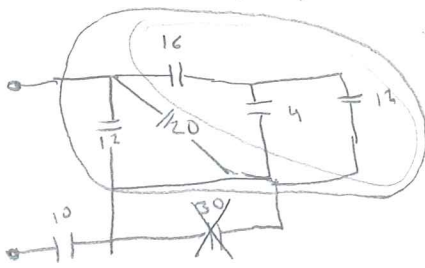


$$\left(\frac{1}{16} + \frac{1}{16}\right)^{-1} = 8$$

$$12 + 20 + 8 = 40$$
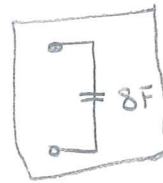
$$\left(\frac{1}{40} + \frac{1}{10}\right)^{-1} = 8F$$



3) find i w/ superpos.

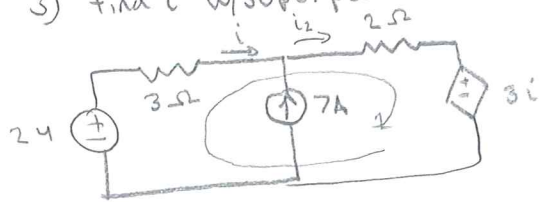


first omit 7A: $24 - 3i - 2i - 3i = 0$
 $24 = 8i \Rightarrow i = 3A$

2nd omit 24V: $3i + 2i_2 + 3i = 0$
 $i_2 = i + 7$

$$\begin{aligned} 6i + 2i + 14 &= 0 \\ 8i &= -14 \\ i &= -1.75 \end{aligned}$$

$i = 1.25A$

4) solve DC steady state current i

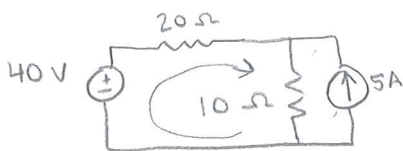

$$40 - 20i - 10(i + 5A) = 0$$

$$-10 - 30i = 0$$

$i = -\frac{1}{3}$

~~$i = 3A$~~

OK $\checkmark$

5) 5mF capacitor $v(t > 0)$ $i(t) = 8\sin(2t) A$ $v(0) = 2V$

$$v_c = v(t_0) + \frac{1}{C} \int_{t_0}^t i dx = 2 + \frac{1}{.005} \int_0^t 8\sin(2t) dt = 2 + 200 \left[-\frac{8}{2} \cos(2t) \right]_0^t$$

$$2 + 200(+4)(1) - 800\cos(2t)$$

$$2 + 800 - 800\cos(2t) V$$

b) find $i(t)$ if $v = 8e^{-4t} V$


$$i_c = C \frac{dv}{dt} = .005(-32e^{-4t}) A$$

$i(t) = -16e^{-4t} A$ $\checkmark$ OK

$v(t) = 802 - 800\cos(2t) V$ $\checkmark$ OK

— Exam 2 —

6) find Thévenin

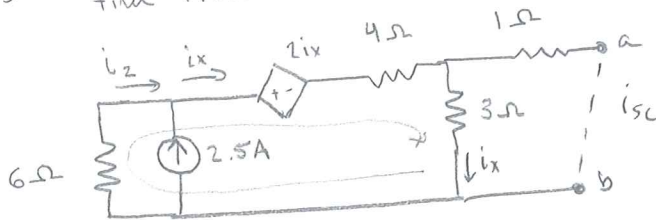

— find V.O.C. $i_2 = i_x - 2.5A$


KVL: $-2i_x - 4i_x - 3i_x - 6i_2 = 0$

$$-9i_x - 6i_x - 15A = 0$$

$$-15i_x = 15A \Rightarrow i_x = -1A$$

$$V_{OC} = 3(-1) = \boxed{-3V}$$

— find I_{SC}

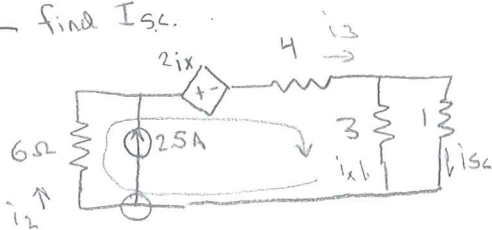

$$-6i_2 - 2i_x - 4i_3 - 3i_x = 0$$

$$-6(-2.5 + 4i_x) - 5i_x - 4(4i_x) = 0$$


$$15 - 45i_x = 0 \Rightarrow i_x = \frac{1}{3}A$$

$$i_2 = i_x - 2.5 + i_{sc} = -2.5 + 4i_x$$

$$i_3 = i_x + i_{sc} = 4i_x$$

$$i_{sc} = 3i_x$$


$$\boxed{i_{sc} = 1A}$$

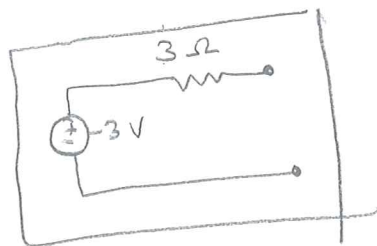

$$i = \frac{V}{R}$$

$$1 = \frac{-3}{R} \quad R = -3$$

7)

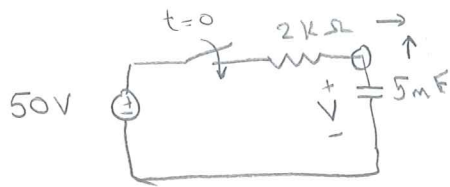 $V(0^+) = 4V$ find $V(t)$ for $t \geq 0$ $V_{max} = ?$


$$i = \frac{V}{R}$$

$$V_C = \frac{1}{C} \int_{t_0}^t i dx$$

KCL

$$C \frac{dV}{dt} + \frac{V - V_S}{R} = 0$$

$$\frac{dV}{dt} + \frac{V}{CR} = \frac{V_S}{CR}$$

$$\frac{dV}{dt} + \frac{1}{10} V = 5$$

$$V_C = K_1 e^{-0.1t}$$

$$V_P = K_2 \quad \frac{1}{10} K_2 = 5$$

$$V_{\infty} = K_2 = 50V$$


initial
condition

$$V(0) = 4 = 50 + K_1 e^{-0.1 \cdot 0}$$

$$-46 = K_1(1)$$

$$K_1 = -46$$

$$V(t) = 50 - 46 e^{-0.1t}$$

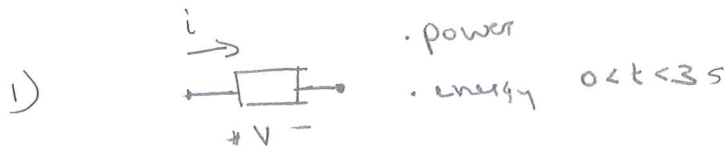

$$i = 2e^{-3t} \text{ A} \quad v = 6e^{-3t} \text{ V}$$


$$P = Vi = 12e^{-3t} e^{-3t} = \boxed{12e^{-6t} \text{ W}}$$

$$E = \int_0^t P dt = \int_0^3 12e^{-6t} dt = 12 \left[\frac{1}{-6} e^{-6t} \right]_0^3$$

$$= -2[e^{-18} - 1] = \boxed{2 \text{ J}}$$

OK


2)

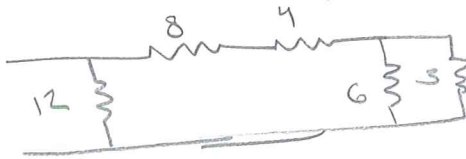

$$\left\{ \left(\frac{1}{6} + \frac{1}{3} \right)^{-1} + 8 + 4 \right\} = 2$$

$$14 \parallel 12 = \boxed{6.46 \Omega} = R_{eq}$$

3)

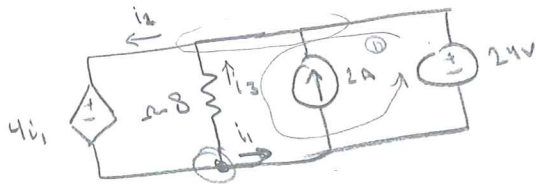find i_2, i_3 KCL

$$i_1 - i_2 + i_3 = 0$$

KVL ①

$$24V + 8i_3 = 0$$

$$i_3 = \frac{-24}{8} = -3$$


$$i_3 = i_2 - i_1$$

$$-3A = i_2 - i_1$$

$$4i_1 = 24V$$

$$\boxed{i_1 = 6A \quad i_2 = 3A}$$

OK ✓

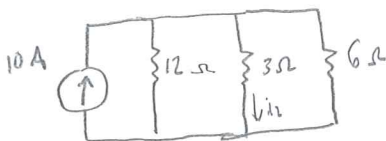4) find i_2 

$$\frac{10A \cdot \frac{1}{3}}{\frac{1}{12} + \frac{1}{3} + \frac{1}{6}}$$


$$= \boxed{5.71A}$$

OK ✓

5) Cu, wire, 10m, $d = 2.6\text{mm}$ resistivity $= 1.7 \times 10^{-8} \Omega \cdot \text{m}$ find resistance

$$R = \frac{1.7 \times 10^{-8} L}{A} = \boxed{.0320 \Omega}$$

6) Solve node voltages V_1, V_2

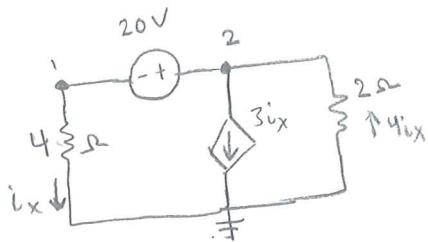

$$V_2 = V_1 + 20$$


$$-20 - 4i_x - 8i_x = 0$$

$$-20 = 12i_x \Rightarrow i_x = -1.67$$

OK ✓

$$V_1 = 4i_x = \boxed{-6.67} \quad \boxed{V_2 = 13.3}$$

7) Set up eqns for mesh.

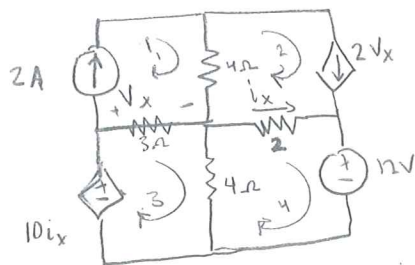

$$i_1 = 2A \quad i_x = i_4 - i_2$$

$$i_2 = 2V_x$$

$$+12 + 4(i_4 - i_3) + 2(i_4 - i_2) = 0$$

$$+4(i_3 - i_4) + 3(i_3 - i_1) - 10(i_4 - i_2) = 0$$

$$+4(i_1 - i_2) + (i_1 - i_3)(3) = 0$$

$$+2(i_2 - i_4) + 4(i_2 - i_1) = 0$$

$$\begin{bmatrix} 0 & -2 & -4 & 6 \\ -3 & 10 & 7 & -14 \\ 7 & -4 & -3 & 0 \\ -4 & 6 & 0 & -2 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} -12 \\ 0 \\ 0 \\ 0 \end{bmatrix} \quad \checkmark$$

$$\begin{bmatrix} 0 & -1 & -2 & 3 \\ -3 & 0 & 7 & 4 \\ 7 & -4 & -3 & 0 \\ -2 & 3 & 0 & -1 \end{bmatrix} \Rightarrow \begin{bmatrix} 12 \\ 0 \\ 0 \\ 0 \end{bmatrix}$$

Name Key

EE 281 A

Exam 2

Spring 2011

Show all your work. Circle or box your answer.

$$V_k = \frac{R_k}{R_1 + R_2 + R_3 + \dots + R_n} V_s$$

$$i_k = \frac{\frac{1}{R_k}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}} i_s$$



$$R = \frac{\rho L}{A}$$

$$i_C = C \frac{dv}{dt} \quad v_C = \frac{1}{C} \int_{-\infty}^t i \, d\lambda = v(t_0) + \frac{1}{C} \int_{t_0}^t i \, d\lambda$$

$$v_L = L \frac{di}{dt} \quad i_L = \frac{1}{L} \int_{-\infty}^t v \, d\lambda = i(t_0) + \frac{1}{L} \int_{t_0}^t v \, d\lambda$$

$$P_{\max} = \frac{v_{th}^2}{4R_{th}}$$

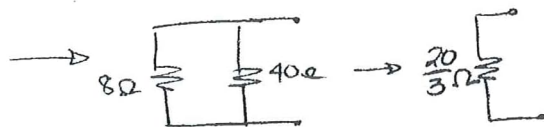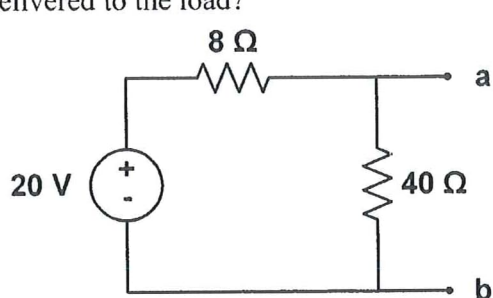
1. What load resistance should be placed between terminals a and b so that maximum power is delivered to the load?





(10 pts)

$$R_{th} = R_{load} = \frac{20}{3} \Omega$$

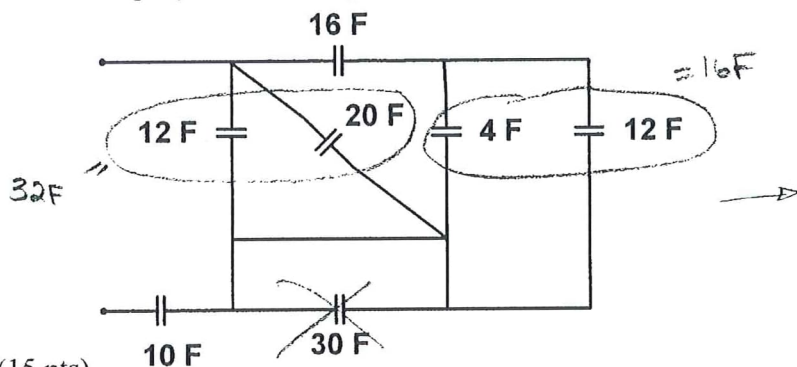
2. Simplify the following to a single equivalent component.



(15 pts)

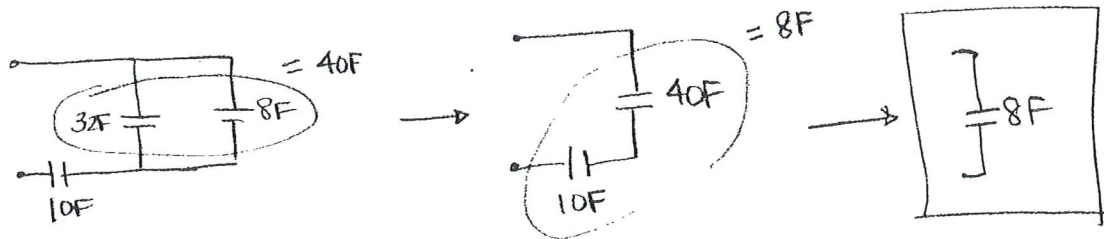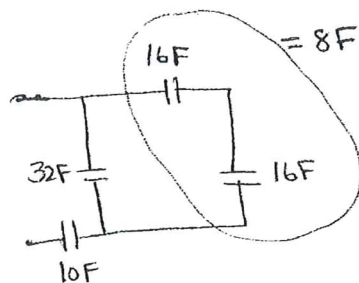


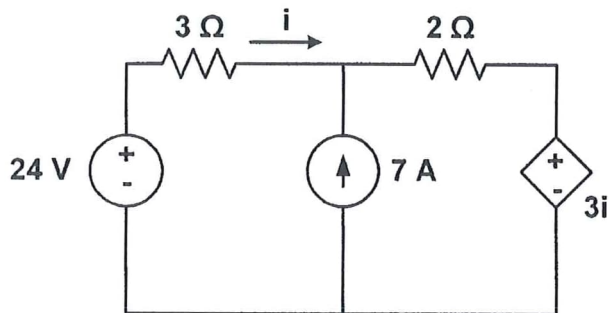3. Use superposition to find i in the following circuit.




(15 pts)

① Keep 24-V source

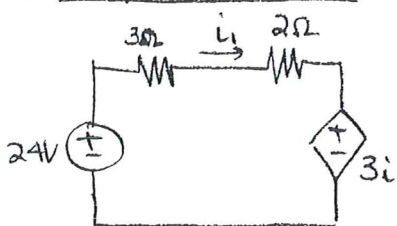

$$\begin{aligned} \text{KVL: } -24 + 3i_1 + 2i_1 + 3i_1 &= 0 \\ 8i_1 &= 24 \\ i_1 &= 3\text{ A} \end{aligned}$$



② Keep 7-A source

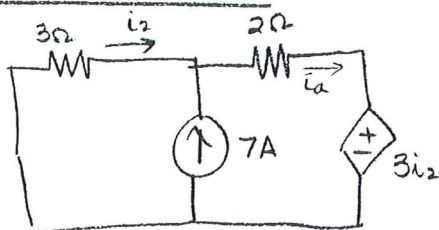

$$\begin{aligned} \text{KCL: } -i_2 + i_a - 7 &= 0 \\ i_a &= 7 + i_2 \\ \text{KVL: } 3i_2 + 2i_a + 3i_2 &= 0 \\ 6i_2 + 2(7 + i_2) &= 0 \\ 8i_2 &= -14 \\ i_2 &= -\frac{14}{8} = -\frac{7}{4}\text{ A} \end{aligned}$$

$$i = i_1 + i_2 = 3 - \frac{7}{4} = \boxed{1.25\text{ A}}$$

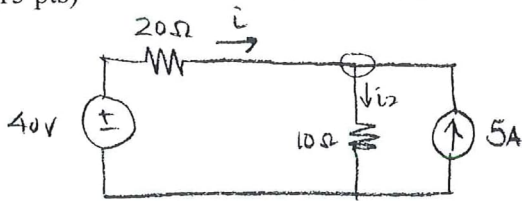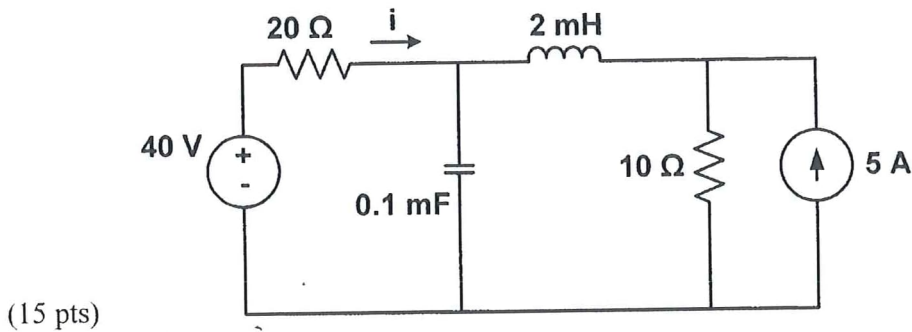4. Solve for the DC steady-state current, i , in the following circuit.



KCL: $i_2 - i - 5 = 0$
 $i_2 = 5 + i$

KVL: $-40 + 20i + 10i_2 = 0$
 $-40 + 20i + 10(5 + i) = 0$
 $30i = -10$ $i = -1/3 \text{ A}$

5. For a 5-mF capacitor, calculate each of the following:
 (10 pts)


- a. The voltage for $t > 0$ across the capacitor if the current through the capacitor is $i(t) = 8 \sin(2t)$ V and the initial voltage across the capacitor is $v(0) = 2$ V.

$$\begin{aligned} V(t) &= V(0) + \frac{1}{C} \int_0^t i \, d\lambda \\ &= 2 + \frac{1}{0.005} \int_0^t 8 \sin(2\lambda) \, d\lambda \\ &= 2 + 200 (-4 \cos(2\lambda)) \Big|_0^t \\ &= 2 + 800(1 - \cos(2t)) = \boxed{802 - 800 \cos(2t) \text{ V}} \end{aligned}$$


- b. The current as a function of time through the capacitor if the voltage across the capacitor is $v(t) = 8e^{-4t}$ V.

$$\begin{aligned} i &= C \frac{dv}{dt} = 0.005 (-32 e^{-4t}) \\ &= \boxed{-0.16 e^{-4t} \text{ A}} \end{aligned}$$

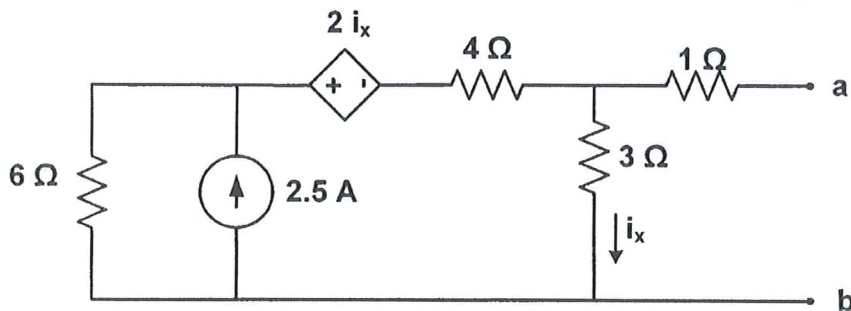6. Find the Thévenin equivalent of the following circuit. Sketch the equivalent circuit.




(20 pts)

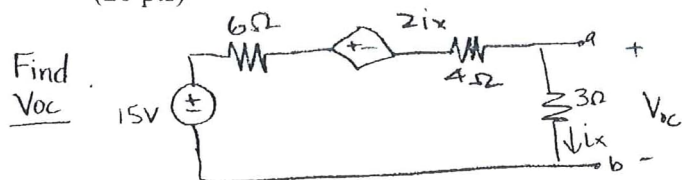

KVL: $-15 + 6i_x + 2i_x + 4i_x + 3i_x = 0$
 $15i_x = 15$
 $i_x = 1$

$V_{oc} = 3i_x = 3V$

7pts

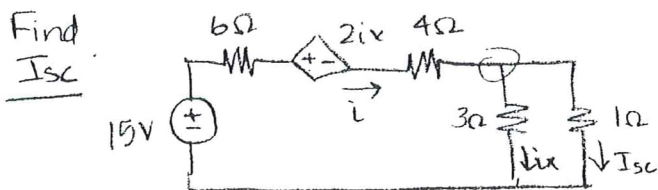

KVL: $-15 + 6i + 2i_x + 4i + 3i_x = 0 \rightarrow 10i + 5i_x = 15$

$i = \frac{15 - 5i_x}{10} = \frac{3 - i_x}{2}$

KCL: $-i + i_x + I_{sc} = 0$

KVL: $3i_x = 1 \cdot I_{sc}$

$\frac{i_x - 3}{2} + i_x + I_{sc} = 0$


$\frac{(I_{sc}/3) - 3}{2} + \frac{I_{sc}}{3} + I_{sc} = 0$

$R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{3V}{1A} = 3\Omega$

3pts


$I_{sc} = \frac{3/2}{1/6 + 1/3 + 1} = 1A$

7pts

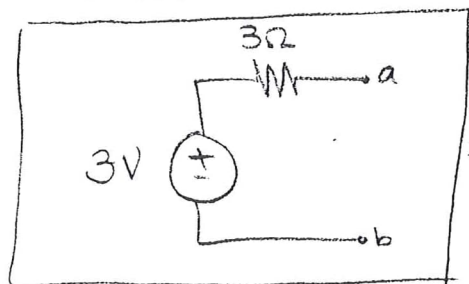

3pts

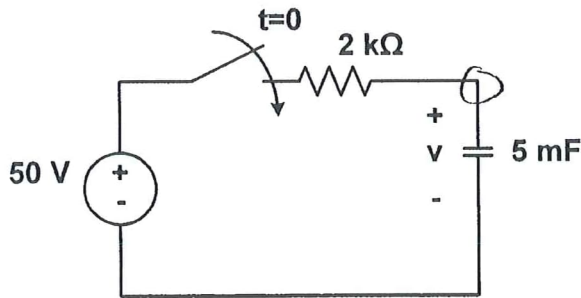7. If the initial voltage across the capacitor is $v(0^+) = 4$ V, find the voltage, $v(t)$, across the capacitor for $t \geq 0$. What is the maximum voltage across the capacitor for $t > 0$?



(15 pts)

KCL: $C \frac{dv}{dt} + \frac{V - V_s}{R} = 0$

$$\frac{dv}{dt} + \frac{1}{RC} V = \frac{1}{RC} V_s$$

$$\frac{dv}{dt} + \frac{1}{10} V = 5$$

$$V_c = K_1 e^{-\frac{1}{10}t}$$

$$V_p = K_2 \leadsto \frac{1}{10} K_2 = 5$$

$$K_2 = 50$$

$$V(t) = K_1 e^{-\frac{1}{10}t} + 50$$

$$V(0) = 4 = K_1 + 50$$

$$K_1 = -46$$

$$V(t) = 50 - 46e^{-\frac{1}{10}t} \text{ V}$$

$$V_{\max} = 50 \text{ V}$$

Practice for final

B

Name Key

EE 281 A

Exam 3

Spring 2011

Show all your work. Circle or box your answer.

$$V_k = \frac{R_k}{R_1 + R_2 + R_3 + \dots + R_n} V_s$$

$$i_k = \frac{\frac{1}{R_k}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}} i_s$$

$$R = \frac{\rho L}{A}$$

$$P_{\max} = \frac{v_{th}^2}{4R_{th}}$$

$$e^{j\omega t} = \cos(\omega t) + j \sin(\omega t)$$

$$i_C = C \frac{dv}{dt} \quad v_C = \frac{1}{C} \int_{-\infty}^t i \, d\lambda = v(t_0) + \frac{1}{C} \int_{t_0}^t i \, d\lambda \quad V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2 dt}$$

$$v_L = L \frac{di}{dt} \quad i_L = \frac{1}{L} \int_{-\infty}^t v \, d\lambda = i(t_0) + \frac{1}{L} \int_{t_0}^t v \, d\lambda$$

$$P = \frac{1}{2} V_m I_m \cos(\theta) = V_{rms} I_{rms} \cos(\theta)$$


$$|S| = \frac{P}{PF} = \frac{1}{2} V_m I_m = V_{rms} I_{rms}$$

$$Q = \frac{1}{2} V_m I_m \sin(\theta) = V_{rms} I_{rms} \sin(\theta)$$

$$x_p = \begin{cases} A \\ Ae^{bt} \\ Ae^{at} \cos(bt) + Be^{at} \sin(bt) \end{cases}$$

$$x_n = \begin{cases} K_1 e^{s_1 t} + K_2 e^{s_2 t} \\ K_1 e^{st} + K_2 t e^{st} \\ K_1 e^{at} \cos(bt) + K_2 e^{at} \sin(bt) \end{cases}$$

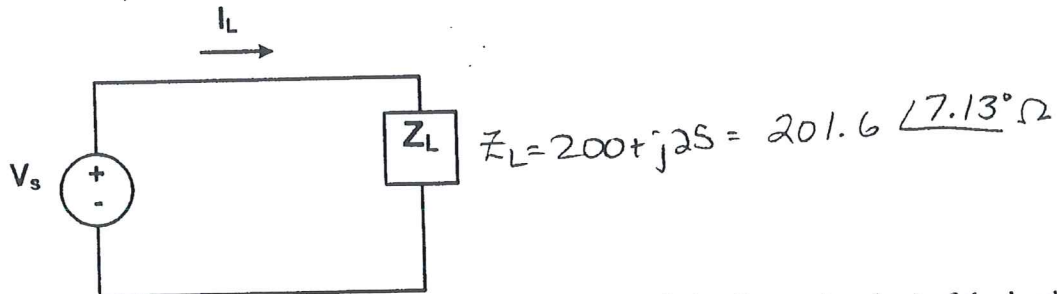1. In the following circuit, the source is a 60-Hz, 20-V_{rms} source and the load consists of a resistor and inductor in series with an impedance of $Z_L = 200 + j25 \Omega$.



- a. Find the power factor (include whether it is leading or lagging) of the load.
(5 pts)
- b. Find the RMS current through the load Z_L . (Note: there will not be an angle associated with this current since you were not given one for the voltage source.)
(5 pts)

$$PF = \cos(7.13^\circ) = \boxed{0.992 \text{ lagging}}$$

$$I_{rms} = \frac{V_{rms}}{|Z_L|} = \frac{20}{201.6} = \boxed{0.099 \text{ A}_{rms}}$$


- c. Calculate the average (real) power absorbed by the load.
(5 pts)

$$P = \frac{1}{2} V_m I_m \cdot PF = V_{rms} I_{rms} \cdot PF = 20(0.099)(0.992) = \boxed{1.96 \text{ W}}$$

- d. Find the apparent power absorbed by the load.
(5 pts)

$$|S| = V_{rms} I_{rms} = 20(0.099) = \boxed{1.98 \text{ VA}}$$

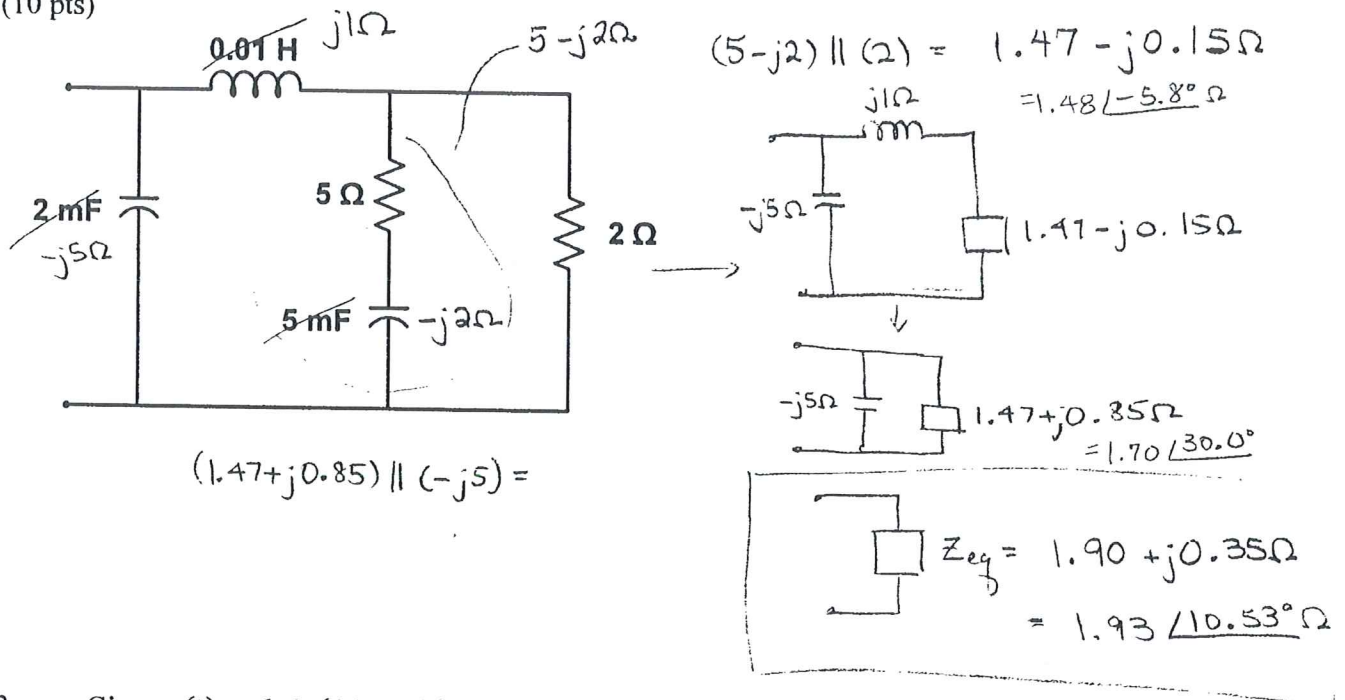2. Find the equivalent impedance, Z_{eq} , of the following. Assume that $\omega = 100$ rad/sec.
(10 pts)



3. Given $v(t) = 6 \sin(14t + 5^\circ)$ V:


- a. Find the RMS value of $v(t)$.
(4 pts)

$$V_{rms} = \frac{6}{\sqrt{2}} = 4.24 V_{rms}$$

- b. Write $v(t)$ as a phasor.
(4 pts)


$$\underline{V} = 6 \angle -85^\circ \text{ V}$$

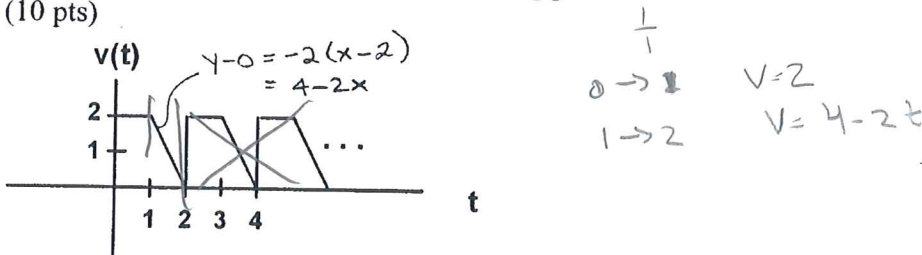4. Find the RMS value of the following period function:
(10 pts)



$$\begin{aligned}
 V_{rms} &= \sqrt{\frac{1}{2} \left(\int_0^1 (2)^2 dt + \int_1^2 (4-2t)^2 dt \right)} \\
 &= \sqrt{\frac{1}{2} \left[(4t) \Big|_0^1 + \frac{(4-2t)^3}{-6} \Big|_1^2 \right]} \\
 &= \sqrt{\frac{1}{2} \left[4 + \frac{8}{6} \right]} = \sqrt{\frac{1}{2} \left(\frac{16}{3} \right)} = \sqrt{\frac{8}{3}} = 1.63 V_{rms}
 \end{aligned}$$

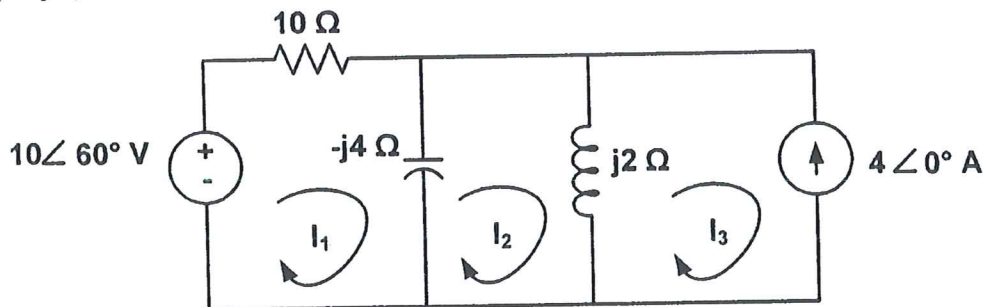5. Set up the equations in matrix form to find the phasor mesh currents I_1 , I_2 , and I_3 in the following circuit. Do not solve.
(12 pts)




m1: $-10\angle 60^\circ + 10I_1 + (-j4)(I_1 - I_2) = 0$
 $(10 - j4)I_1 + j4I_2 = 10\angle 60^\circ$

m2: $-j4(I_2 - I_1) + j2(I_2 - I_3) = 0$
 $j4I_1 + (-j2)I_2 - j2I_3 = 0$

m3: $I_3 = -4\angle 0^\circ$

$$\begin{bmatrix} 10-j4 & j4 & 0 \\ j4 & -j2 & -j2 \\ 0 & 0 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 10\angle 60^\circ \\ 0 \\ -4\angle 0^\circ \end{bmatrix}$$

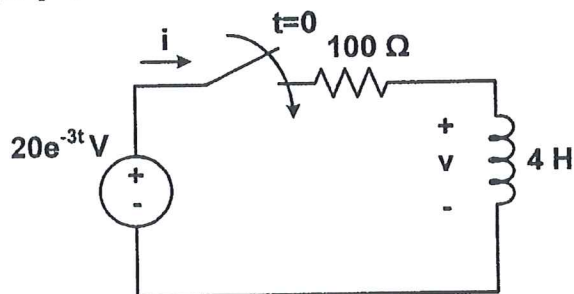6. Find the current, $i(t)$, for $t > 0$ in the following circuit. Solve for all the constants.
(15 pts)



KVL: $-20e^{-3t} + 100i + 4 \frac{di}{dt} = 0$ (3 pts)

$$\frac{di}{dt} + 25i = 5e^{-3t}$$

$\lambda + 25 = 0 \rightarrow i_c(t) = K_1 e^{-25t}$ (4 pts)

$i_p(t) = A e^{-3t}$

$i_p' = -3A e^{-3t}$

$-3A e^{-3t} + 25A e^{-3t} = 5e^{-3t}$

$22A = 5 \rightarrow A = 5/22$


$i(t) = K_1 e^{-25t} + \frac{5}{22} e^{-3t}$

3 pts $i(0) = 0 = K_1 + 5/22 \rightarrow K_1 = -5/22$

1 pt $i(t) = \frac{5}{22} e^{-3t} - \frac{5}{22} e^{-25t} \text{ A}$

$= 0.23e^{-3t} - 0.23e^{-25t} \text{ A}$

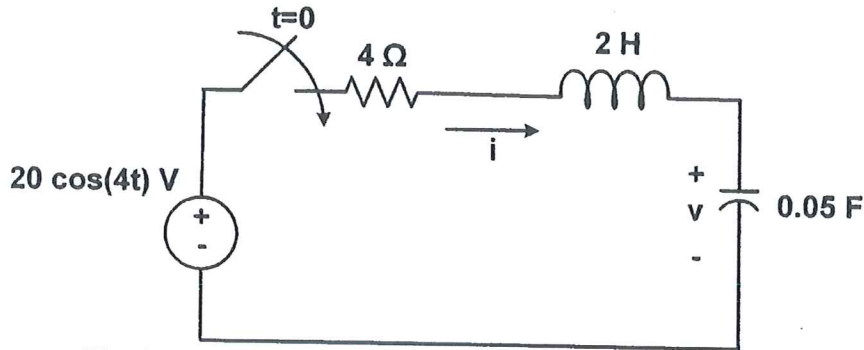7. Assuming that $v(0^+) = 0$, use the circuit below to find:



- a. The form of the source-free (natural) solution of $i(t)$.
(10 pts)

$$-20 \cos(4t) + 4i + 2 \frac{di}{dt} + \frac{1}{0.05} \int_{-\infty}^t i d\lambda = 0$$

$$\frac{d^2 i}{dt^2} + 2 \frac{di}{dt} + 10i = -40 \sin(4t)$$

$$\lambda^2 + 2\lambda + 10 = 0$$

$$\lambda = \frac{-2 \pm \sqrt{4 - 4(10)}}{2} = -1 \pm j3$$

$$i_c(t) = K_1 e^{-t} \cos(3t) + K_2 e^{-t} \sin(3t)$$

- b. The steady-state (particular) solution of $i(t)$.
(8 pts)

$$\begin{aligned} -6A + 8B &= 0 \Rightarrow B = \frac{3}{4}A \\ -8A - 6B &= -40 \\ \left(-8 - 6\left(\frac{3}{4}\right)\right)B &= -40 \end{aligned}$$

$$B = 3.2$$

$$A = 2.4$$

$$i_p(t) = A \cos(4t) + B \sin(4t)$$

$$i_p' = -4A \sin(4t) + 4B \cos(4t)$$

$$i_p'' = -16A \cos(4t) - 16B \sin(4t)$$

$$\frac{-16A \cos(4t) - 16B \sin(4t) - 8A \sin(4t) + 8B \cos(4t) + 10A \cos(4t) + 10B \sin(4t)}{\cos(4t)(-6A + 8B) + \sin(4t)(-6B - 8A)} = -40 \sin(4t)$$

$$\cos(4t)(-6A + 8B) + \sin(4t)(-6B - 8A) = -40 \sin(4t)$$

$$i_p(t) = 2.4 \cos(4t) + 3.2 \sin(4t)$$

- c. The other initial conditions: $i(0^+)$ and $\frac{di}{dt}|_{t=0^+}$.
(4 pts)

$$i(0^+) = 0 \text{ A}$$

$$\text{KVL: } -20 + 4i(0) + 2 \frac{di}{dt}|_{t=0} + v(0) = 0 \Rightarrow \frac{di}{dt}|_{t=0} = 10$$

- d. Is this circuit overdamped, underdamped, or critically damped?
(3 pts)

Practice for final

Name

Key

B

EE 281 A

Exam 1

Spring 2011

Show all your work. Circle or box your answer.

$$v_k = \frac{R_k}{R_1 + R_2 + R_3 + \dots + R_n} v_s$$

$$i_k = \frac{\frac{1}{R_k}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}} i_s$$


$$R = \frac{\rho L}{A}$$

• Sean

— Lindsey

Chaffin

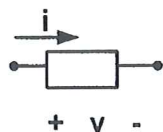1. Calculate the power absorbed by the circuit element as a function of time. Calculate the energy delivered to the element on the interval $0 \leq t < 3$ s.



$$i = 2e^{-3t} \text{ A}$$

$$v = 6e^{-3t} \text{ V}$$



(10 pts)

$$p(t) = iv = (2e^{-3t})(6e^{-3t}) = \boxed{12e^{-6t} \text{ W}}$$

$$W(t) = \int_0^3 p(t) dt = \int_0^3 12e^{-6t} dt = \left. \frac{12}{-6} e^{-6t} \right|_0^3 = -2(e^{-18} - 1) \approx \boxed{2.0 \text{ J}}$$

2. Simplify the following to a single equivalent resistance.

(15 pts)

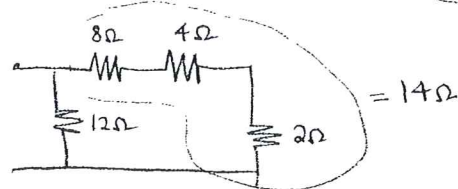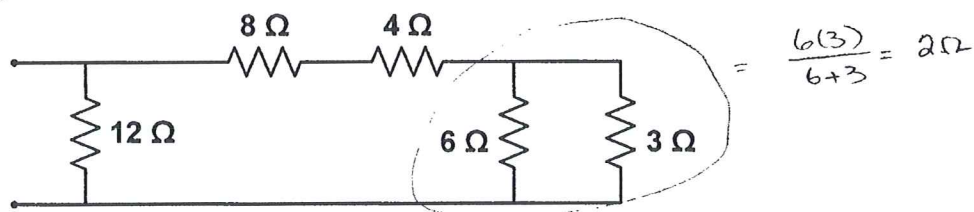

$$\text{Final simplified circuit: } 12 \Omega \parallel 14 \Omega = \frac{12(14)}{12+14} = \frac{168}{26} = \boxed{6.46 \Omega}$$

5. Calculate the resistance of a 10-m long piece of copper wire that has a diameter of 2.6 mm. The resistivity of copper is $1.7 \times 10^{-8} \Omega \cdot \text{m}$.


(10 pts)

$$R = \frac{\rho l}{A} = \frac{(1.7 \times 10^{-8} \Omega \cdot \text{m})(10 \text{ m})}{\pi (1.3 \times 10^{-3})^2} = \boxed{0.032 \Omega}$$

$$= 32 \text{ m}\Omega$$

6. Solve for the node voltages, v_1 and v_2 , in the following circuit.

(15 pts)

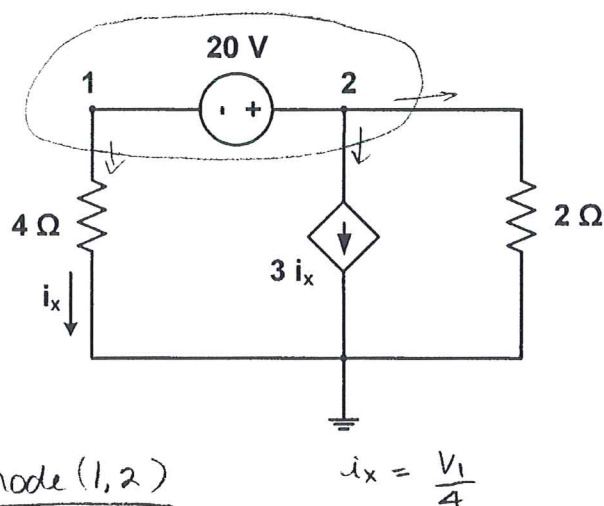

Super node (1, 2)

$$\textcircled{1} \quad v_2 - v_1 = 20 \text{ V}$$

KCL: $\frac{v_1}{4} + 3i_x + \frac{v_2}{2} = 0$

$$\frac{v_1}{4} + 3\left(\frac{v_1}{4}\right) + \frac{v_2}{2} = 0$$

$$\textcircled{2} \quad v_1 + \frac{1}{2}v_2 = 0$$

$$\boxed{\begin{aligned} v_1 &= -\frac{20}{3} \text{ V} = -6.67 \text{ V} \\ v_2 &= \frac{40}{3} \text{ V} = 13.33 \text{ V} \end{aligned}}$$

$$-v_1 + v_2 = 20$$

$$v_1 + \frac{1}{2}v_2 = 0$$


$$\frac{3}{2}v_2 = 20$$

$$v_2 = \frac{40}{3}$$

$$v_1 = -\frac{1}{2}v_2$$

$$v_1 = -\frac{20}{3}$$

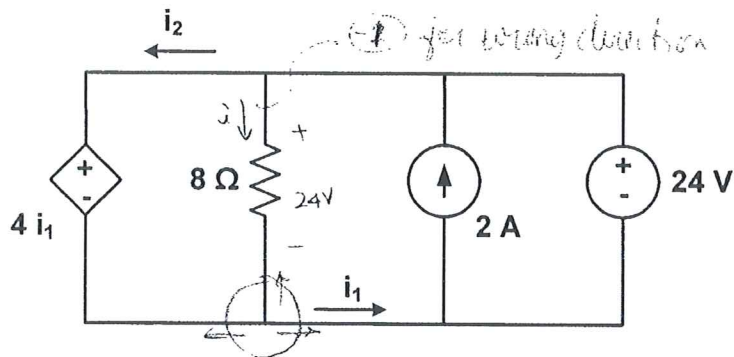3. Solve for i_1 and i_2 in the following circuit.
(15 pts)



KVL outer loop

$$4i_1 = 24$$

$$i_1 = 6A$$

$$i = \frac{24}{8} = 3A$$


KCL bottom node

$$-i_2 - 3 + i_1 = 0$$

$$i_2 = i_1 - 3 = 6 - 3 = 3$$


$$i_2 = 3A$$

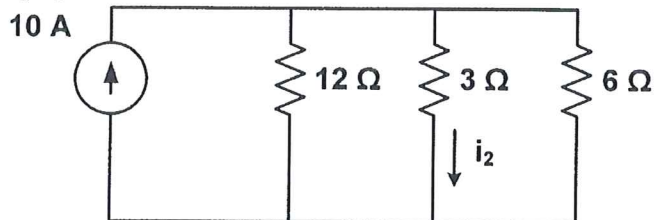4. Use current divider to find i_2 in the following circuit.
(10 pts)



$$i_2 = \frac{\frac{1}{3}}{\frac{1}{12} + \frac{1}{3} + \frac{1}{6}} (10A) = \frac{\frac{10}{3}}{\frac{7}{12}} = \frac{40}{7} A$$

7. Set up the equations to find the mesh currents, i_1 , i_2 , i_3 , and i_4 , in the following circuit in matrix form. You must eliminate the control variables, v_x and i_x , from your equations. (25 pts)

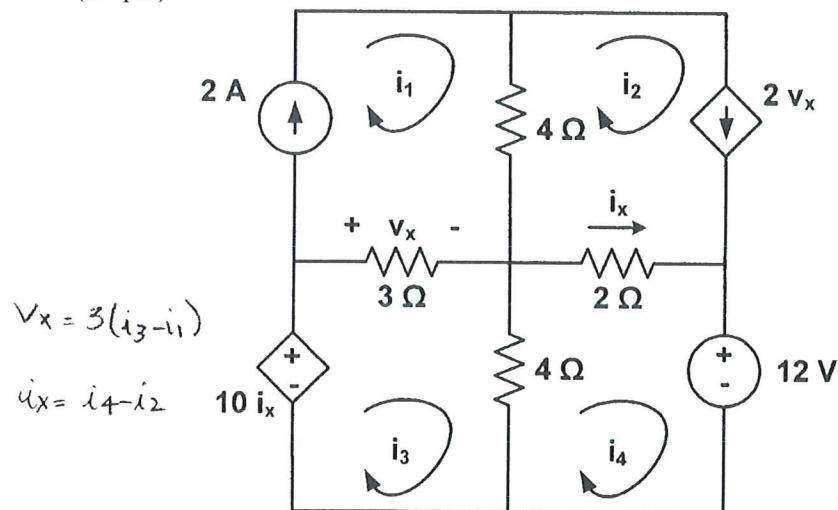

mesh 1:

① $i_1 = 2A$

mesh 2:

$i_2 = 2v_x = 6(i_3 - i_1)$

② $6i_1 + i_2 - 6i_3 = 0$

mesh 3

$-10i_x + 3(i_3 - i_1) + 4(i_3 - i_4) = 0$

$-10(i_4 - i_2) + 7i_3 - 3i_1 - 4i_4 = 0$

③ $-3i_1 + 10i_2 + 7i_3 - 14i_4 = 0$

mesh 4

$4(i_4 - i_3) + 2(i_4 - i_2) + 12 = 0$

$-2i_2 - 4i_3 + 6i_4 = -12$

$$\begin{bmatrix} 1 & 0 & 0 & 0 \\ 6 & 1 & -6 & 0 \\ -3 & 10 & 7 & -14 \\ 0 & -2 & -4 & 6 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} 2 \\ 0 \\ 0 \\ -12 \end{bmatrix}$$

Practice for final

Name Key


EE 281 B

Exam 4

Fall 2010

Show all your work. Circle or box your answer.

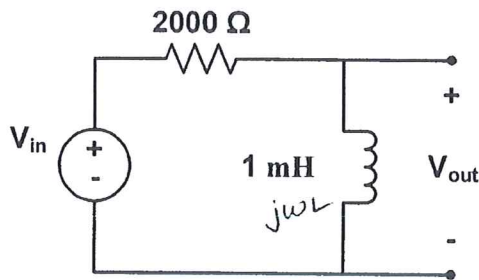1. Find the transfer function $H(j\omega) = \frac{V_{out}}{V_{in}}$ for the following filter. Is this a highpass or lowpass filter?




$$H(j\omega) = \frac{j\omega L}{R + j\omega L} = \frac{j\omega(0.001)}{2000 + j\omega(0.001)}$$

high pass

(15 pts)

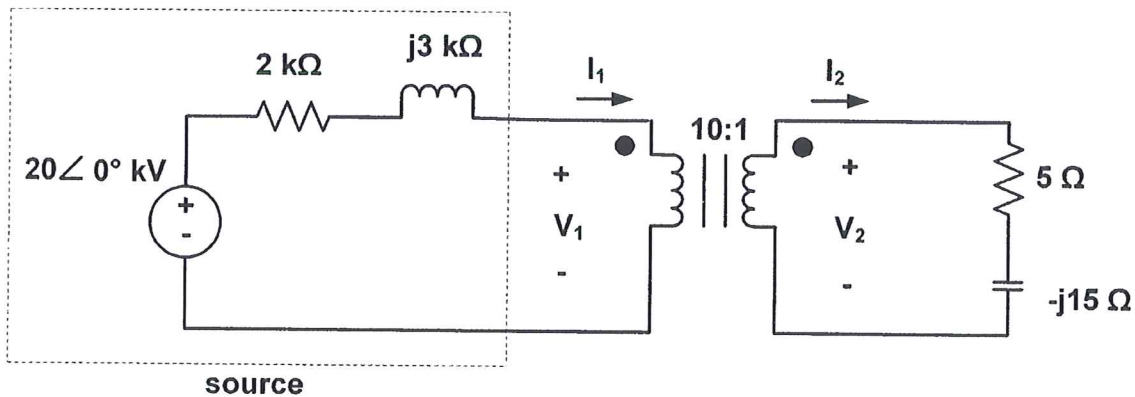2. Using impedance transformations (reflected impedances), find the equivalent impedance seen by the source in the following circuit.




(10 pts) $Z_L' = \left(\frac{N_1}{N_2}\right)^2 Z_L = \left(\frac{10}{1}\right)^2 (5 - j15) = 500 - j1500 \Omega$

3. Find the turns ratio of an ideal transformer necessary to step a 40-V_{rms} source up to 1000 V_{rms}.

(5 pts) $\frac{V_2}{V_1} = \frac{N_2}{N_1} = \frac{1000}{40} = \frac{25}{1}$

$N_1 : N_2 = 1 : 25$

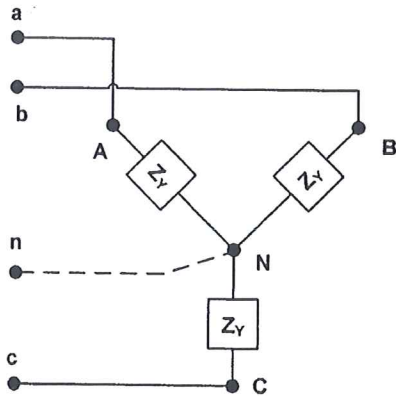4. A balanced Y-connected load has an impedance of $Z_Y = 300 + j20 \Omega$ for each phase. Assuming the phase sequence is positive and that V_{AB} is the reference, find the following when the line voltage is $V_L = 20 \text{ kV}_{\text{rms}}$.



$$Z_Y = 300 + j20 \Omega = 300.67 \angle 3.81^\circ \Omega$$

$$V_{AB} = 20 \angle 0^\circ \text{ kV}_{\text{rms}}$$

$$V_L = V_Y$$

- a. The phasor line-to-neutral voltage V_{AN} .

(3 pts)

$$V_{AN} = \frac{V_{AB}}{\sqrt{3} \angle 30^\circ} = \frac{20 \angle -30^\circ}{\sqrt{3}} \text{ V}_{\text{rms}}$$

- b. The phasor currents I_{AN} , I_{BN} , and I_{CN} .

(9 pts)

$$I_{AN} = \frac{V_{AN}}{Z_Y} = \frac{20,000/\sqrt{3} \angle -30^\circ}{300 + j20} = 38.40 \angle -33.8^\circ \text{ A}$$

$$I_{BN} = 38.40 \angle -153.8^\circ \text{ A}$$

$$I_{CN} = 38.40 \angle -273.8^\circ \text{ A}$$

- c. The phasor line current I_{aA} .

(5 pts)

$$I_{aA} = I_{AN} = 38.40 \angle -33.8^\circ \text{ A}$$

- d. The average power, P , absorbed by the 3-phase load.

(5 pts)

$$P = 3 V_Y I_L \cos \theta = 3 \left(\frac{20,000}{\sqrt{3}} \right) (38.4) \cos(3.81^\circ) = 1,327,275 \text{ W}$$

- e. The impedance Z_Δ to create an equivalent Δ -connected load.

(3 pts)

$$Z_\Delta = 3 Z_Y = 900 + j60 \Omega$$

5. The transfer function for a particular first order filter is $H(j\omega) = \frac{V_{out}}{V_{in}} = \frac{j\omega(0.005)}{1+j\omega(0.005)}$

- a. Find the half-power frequency of this filter.
(5 pts)

$$\omega = \frac{1}{0.005} = 200 \text{ rad/sec}$$

$$H(j\omega) = \frac{1}{\sqrt{2}}$$

- b. Find the output current, $v_{out}(t)$ if the input current is $v_{in}(t) = 20 \cos(20t) + 20 \cos(5000t - 45^\circ) \text{ V}$.

(10 pts)

$$\omega = 20 \quad V_{in} = 20 \angle 0^\circ$$



$$V_{out} = \frac{j(20)(0.005)}{1+j(20)(0.005)} 20 \angle 0^\circ = 1.99 \angle 84.3^\circ$$

$$\omega = 5000 \quad V_{in} = 20 \angle -45^\circ$$

$$V_{out} = \frac{j(5000)(0.005)}{1+j(5000)(0.005)} 20 \angle -45^\circ = 19.98 \angle -42.7^\circ$$

$$v_{out}(t) = 1.99 \cos(20t + 84.3^\circ) + 19.93 \cos(5000t - 42.7^\circ) \text{ V}$$

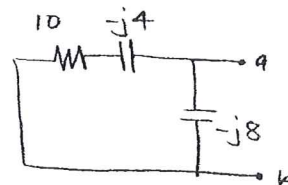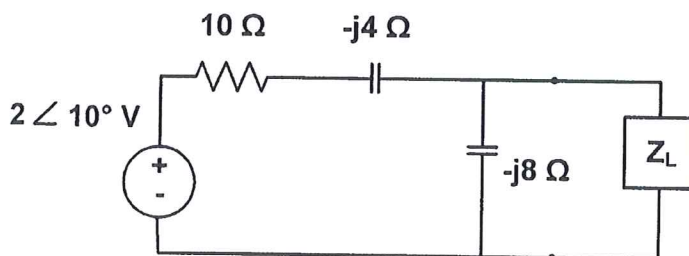6. For the following circuit, determine the value of Z_L that results in maximum average power transferred to Z_L .




(10 pts)

$$Z_{Th} = (10 - j4) \parallel -j8 = \frac{(10 - j4)(-j8)}{10 - j4 - j8} = 5.52 \angle -61.6^\circ \Omega$$


$$= 2.62 - j4.85 \Omega$$

$$Z_L = Z_{Th}^* = 2.62 + j4.85 \Omega$$

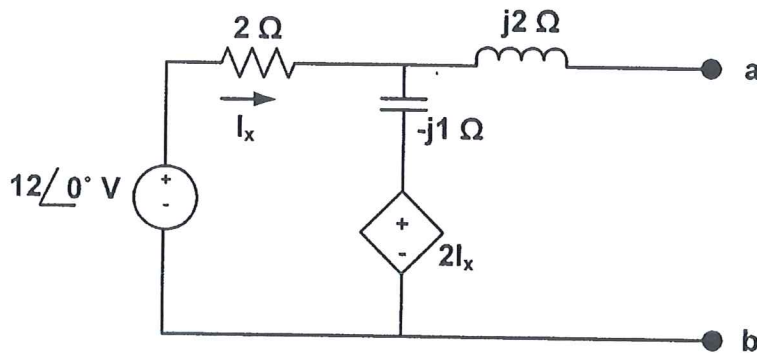7. Find the Thévenin equivalent of the following circuit.



(20 pts)

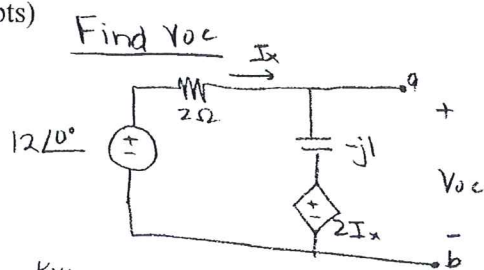



KVL:

$$-12 + 2I_x - jI_x + 2I_x = 0$$

$$(4-j)I_x = 12$$

$$I_x = 12 / (4-j) = 2.91 \angle 14.04^\circ$$
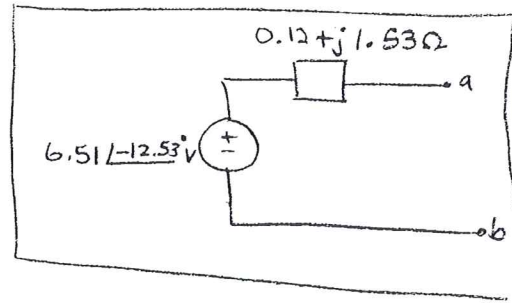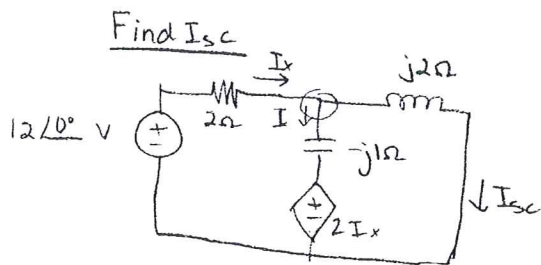
$$V_{oc} = -jI_x + 2I_x = (2-j)I_x = 6.51 \angle -12.53^\circ \text{ V}$$



KVL outer loop: $-12 + 2I_x + j2I_{sc} = 0$

① $2I_x + j2I_{sc} = 12 \Rightarrow I_x = \frac{12 - j2I_{sc}}{2} = 6 - jI_{sc}$

KCL: $I = I_x - I_{sc}$

KVL left loop: $-12 + 2I_x - jI + 2I_x = 0$

$$-12 + 4I_x - j(I_x - I_{sc}) = 0$$

$$Z_{th} = \frac{V_{oc}}{I_{sc}} = \frac{6.51 \angle -12.53^\circ}{4.24 \angle -98.13^\circ}$$

$$= 1.53 \angle 85.6^\circ \Omega$$

$$= 0.12 + j1.53 \Omega$$

$$I_{sc} = \frac{12 - 6(4-j)}{-j(4-j) + j} = -0.6 - j4.2 = 4.24 \angle -98.13^\circ \text{ A}$$

Spacer

Name Key


EE 281 B

Exam 4

Fall 2010

Show all your work. Circle or box your answer.

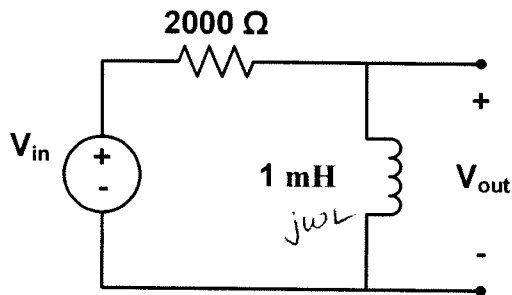1. Find the transfer function $H(j\omega) = \frac{V_{out}}{V_{in}}$ for the following filter. Is this a highpass or lowpass filter?




$$H(j\omega) = \frac{j\omega L}{R + j\omega L} = \frac{j\omega(0.001)}{2000 + j\omega(0.001)}$$

high pass

(15 pts)

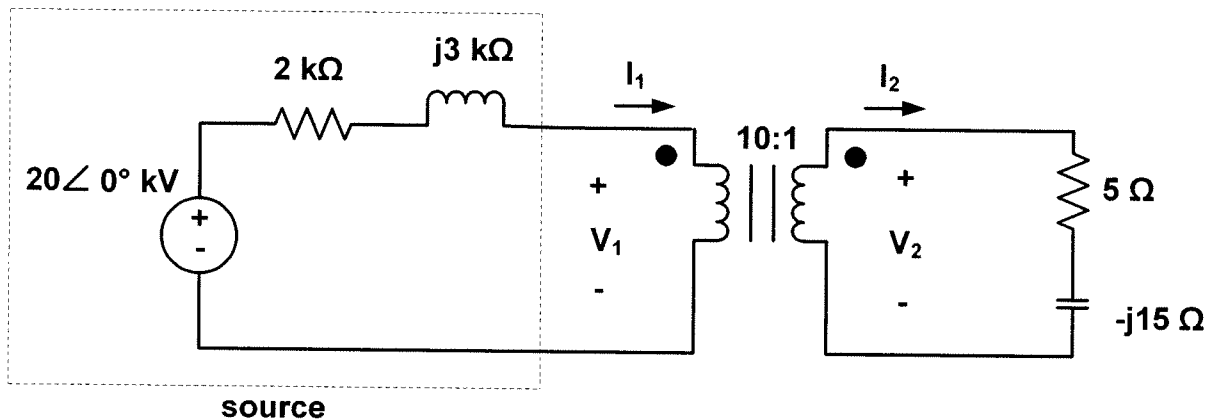2. Using impedance transformations (reflected impedances), find the equivalent impedance seen by the source in the following circuit.




(10 pts) $Z_L' = \left(\frac{N_1}{N_2}\right)^2 Z_L = \left(\frac{10}{1}\right)^2 (5 - j15) = 500 - j1500 \Omega$

3. Find the turns ratio of an ideal transformer necessary to step a 40-V_{rms} source up to 1000 V_{rms}.

(5 pts) $\frac{V_2}{V_1} = \frac{N_2}{N_1} = \frac{1000}{40} = \frac{25}{1}$

$N_1 : N_2 = 1 : 25$

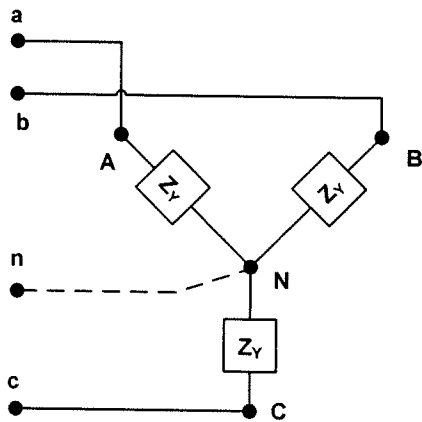4. A balanced Y-connected load has an impedance of $Z_Y = 300 + j20 \Omega$ for each phase. Assuming the phase sequence is positive and that V_{AB} is the reference, find the following when the line voltage is $V_L = 20 \text{ kV}_{\text{rms}}$.



$$Z_Y = 300 + j20 \Omega = 300.67 \angle 3.81^\circ \Omega$$

$$V_{AB} = 20 \angle 0^\circ \text{ kV}_{\text{rms}}$$

- a. The phasor line-to-neutral voltage V_{AN} .

(3 pts)

$$V_{AN} = \frac{V_{AB}}{\sqrt{3} \angle 30^\circ} = \frac{20 \angle -30^\circ}{\sqrt{3}} \text{ V}_{\text{rms}}$$

- b. The phasor currents I_{AN} , I_{BN} , and I_{CN} .

(9 pts)

$$I_{AN} = \frac{V_{AN}}{Z_Y} = \frac{20,000/\sqrt{3} \angle -30^\circ}{300 + j20} = 38.40 \angle -33.8^\circ \text{ A}$$

$$I_{BN} = 38.40 \angle -153.8^\circ \text{ A}$$

$$I_{CN} = 38.40 \angle -273.8^\circ \text{ A}$$

- c. The phasor line current I_{aA} .

(5 pts)

$$I_{aA} = I_{AN} = 38.40 \angle -33.8^\circ \text{ A}$$

- d. The average power, P , absorbed by the 3-phase load.

(5 pts)

$$P = 3 V_Y I_L \cos \theta = 3 \left(\frac{20,000}{\sqrt{3}} \right) (38.4) \cos(3.81^\circ) = 1,327,275 \text{ W}$$

- e. The impedance Z_Δ to create an equivalent Δ -connected load.

(3 pts)

$$Z_\Delta = 3 Z_Y = 900 + j60 \Omega$$

5. The transfer function for a particular first order filter is $H(j\omega) = \frac{V_{out}}{V_{in}} = \frac{j\omega(0.005)}{1+j\omega(0.005)}$.

a. Find the half-power frequency of this filter.
(5 pts)

$$\omega = \frac{1}{0.005} = \boxed{200 \text{ rad/sec}}$$

b. Find the output current, $v_{out}(t)$ if the input current is $v_{in}(t) = 20 \cos(20t) + 20 \cos(5000t - 45^\circ)$ V.
(10 pts)

$$\omega = 20 \quad V_{in} = 20 \angle 0^\circ$$



$$V_{out} = \frac{j(20)(0.005)}{1+j(20)(0.005)} 20 \angle 0^\circ = 1.99 \angle 84.3^\circ$$

$$\omega = 5000 \quad V_{in} = 20 \angle -45^\circ$$

$$V_{out} = \frac{j(5000)(0.005)}{1+j(5000)(0.005)} 20 \angle -45^\circ = 19.98 \angle -42.7^\circ$$

$$\boxed{v_{out}(t) = 1.99 \cos(20t + 84.3^\circ) + 19.98 \cos(5000t - 42.7^\circ) \text{ V}}$$

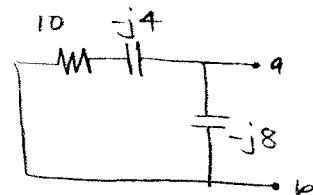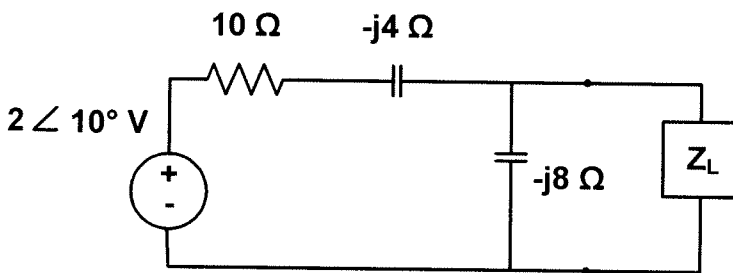6. For the following circuit, determine the value of Z_L that results in maximum average power transferred to Z_L .



(10 pts)

$$Z_{Th} = (10 - j4) \parallel -j8 = \frac{(10 - j4)(-j8)}{10 - j4 - j8} = 5.52 \angle -61.6^\circ \Omega$$

$$= 2.62 - j4.85 \Omega$$

$$\boxed{Z_L = Z_{Th}^* = 2.62 + j4.85 \Omega}$$

Exam 4

Formula Sheet - EE 281

$$V_k = \frac{R_k}{R_1 + R_2 + R_3 + \dots + R_n} V_s$$

$$i_k = \frac{\frac{1}{R_k}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}} i_s$$

$$R = \frac{\rho L}{A}$$

$$P_{\max} = \frac{v_{th}^2}{4R_{th}}$$

$$i_C = C \frac{dv}{dt}$$

$$v_L = L \frac{di}{dt}$$

$$e^{j\omega t} = \cos(\omega t) + j \sin(\omega t)$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2 dt}$$

$$P = \frac{1}{2} V_m I_m \cos(\theta) = V_{rms} I_{rms} \cos(\theta)$$

$$Q = \frac{1}{2} V_m I_m \sin(\theta) = V_{rms} I_{rms} \sin(\theta)$$

$$x_n = \begin{cases} K_1 e^{s_1 t} + K_2 e^{s_2 t} \\ K_1 e^{st} + K_2 t e^{st} \\ K_1 e^{at} \cos(bt) + K_2 e^{at} \sin(bt) \end{cases}$$

$$\omega = 2\pi f$$

$$V_{ab} = V_{an} - V_{bn} = V_{an} \sqrt{3} \angle 30^\circ$$

$$P = 3 V_{Yrms} I_{Lrms} \cos \theta = \frac{3 V_Y I_L}{2} \cos \theta$$

$$V_2 = \frac{N_2}{N_1} V_1$$

$$I_2 = \frac{N_1}{N_2} I_1$$

$$Z'_L = \left(\frac{N_1}{N_2} \right)^2 Z_L$$

Maximize P, $Z_L = Z_{th}^*$

RMS of any sine wave = $\frac{a}{\sqrt{2}}$

$$P_{avg} = I_{rms}^2 R$$

$$V_L = |V_{ab}|$$

$$= |V_{bc}|$$

$$= |V_{ca}|$$

$$\begin{array}{c} L \quad H \\ \text{---} \text{---} \text{---} \text{---} \text{---} \text{---} \\ C \\ \text{---} \text{---} \text{---} \text{---} \text{---} \text{---} \\ -j \\ \omega C \end{array} = L j \omega$$

$$v_C = \frac{1}{C} \int_{-\infty}^t i \, d\lambda = v(t_0) + \frac{1}{C} \int_{t_0}^t i \, d\lambda$$

$$i_L = \frac{1}{L} \int_{-\infty}^t v \, d\lambda = i(t_0) + \frac{1}{L} \int_{t_0}^t v \, d\lambda$$

$$AP = \frac{P}{PF} = \frac{1}{2} V_m I_m = V_{rms} I_{rms}$$


$$x_p = \begin{cases} A \\ A e^{bt} \\ A e^{at} \cos(bt) + B e^{at} \sin(bt) \end{cases}$$

$$Z_\Delta = 3 Z_Y$$

$$I_{aA} = I_{AB} - I_{CA} = I_{AB} \sqrt{3} \angle -30^\circ$$

$$\text{reactive} \Rightarrow Q = 3 V_{Yrms} I_{Lrms} \sin \theta = \frac{3 V_Y I_L}{2} \sin \theta$$

Things to know for Exam 3 — EE 281 —

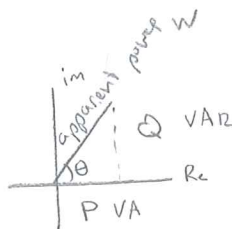

Power factor = $\cos \theta$

O.D.E.

Volt source

$$C \frac{dV}{dt} + \frac{V - V_s}{R} = 0$$

RMS of a cosine/sine = $\frac{\text{Amplitude}}{\sqrt{2}}$

$P = I_{rms}^2 R$ average power = $\frac{V_{rms}^2}{R}$

$Q = I_{rms}^2 X$ reactive power = $\frac{V_{rms}^2}{X}$

$AP = \frac{P}{PF} = \frac{P}{\cos \theta} = \sqrt{P^2 + Q^2}$


$\frac{1}{C} = \frac{1}{j\omega C}$ $\frac{1}{L} = j\omega L$

$200 \cos(200t + 90^\circ) V \Rightarrow 2 \angle 90^\circ V$




$1 \mu F = \frac{1}{1 \times 10^{-6} \times 200} = 5000 \Omega$

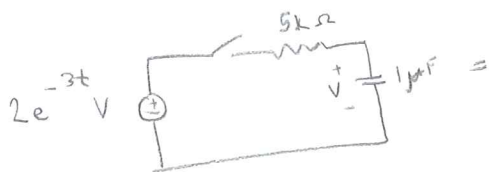$V_{ss} = \frac{-j5000}{5000 - j5000} (2 \angle 90^\circ) = 1.414 \angle -135^\circ V$
 $= 1.414 \cos(200t - 135^\circ)$



$2 \cos(3t + 0)$ $5000 + \frac{1}{1 \times 10^{-6}} \int_{-\infty}^t i dx = 2e^{-3t}$

imaginary current

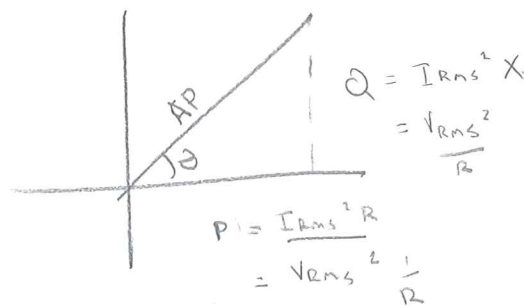

$PF = \cos \theta$